

Chapter 2: Combinational of Boolean Functions

2-8 DIGITAL LOGIC GATES

- Of the 16 function, only eight are considered for gates.
- These are: complement, transfer, AND, OR, NAND, NOR, exclusive-OR, and equivalence
- The graphic symbols and truth tables of the eight gates are shown in Fig 2-5.
- Each gate has only one or two binary input variables designated by x and y.
- Each gate has one binary output variable designated by F.









Name	Graphic symbol	Algebraic function	Truth table															
AND		$F = xy$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	0	0	1	0	1	0	0	1	1	1
x	y	F																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$F = x + y$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	1
x	y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
Inverter		$F = x'$	<table><tr><th>x</th><th>F</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	x	F	0	1	1	0									
x	F																	
0	1																	
1	0																	
Buffer		$F = x$	<table><tr><th>x</th><th>F</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	x	F	0	0	1	1									
x	F																	
0	0																	
1	1																	
NAND		$F = (xy)'$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	1	0	1	1	1	0	1	1	1	0
x	y	F																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR		$F = (x + y)'$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	0
x	y	F																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
Exclusive-OR (XOR)		$F = xy' + x'y$ $= x \oplus y$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	0
x	y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
Exclusive-NOR or equivalence		$F = xy + x'y'$ $= x \odot y$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	1
x	y	F																
0	0	1																
0	1	0																
1	0	0																
1	1	1																

FIGURE 2-5
Digital logic gates

- The inverter circuit inverts the logic sense of a binary variable.
- It produces the NOT, or complement, function.
- The small circle in the output of the graphic symbol of an inverter designates the logic complement.
- The triangle symbol by itself designates a buffer circuit.
- A buffer produces the transfer function but does not produce any particular logic operation.
- The binary value of the output is equal to the binary value of the input.
- This circuit is mainly used for power amplification and is equivalent to two inverters connected in cascade.
- The NAND function is the complement of the AND function.

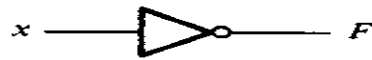- The NAND function is indicated by a graphic symbol that consists of AND graphic symbol followed by a small circle.
- The NOR function is the complement of the OR function and uses an OR graphic symbol followed by a small circle.
- The exclusive –OR gate has a graphic symbol similar to that of the OR gate.
- It has an additional curved line on the input side.
- The equivalence, or exclusive-NOR gate is the complement of the exclusive-OR.
- You can see the small on the output side of the graphic symbol to indicate complement.

Extension to Multiple Inputs

- The gates shown in Fig 2-5, except for the inverter and buffer, can be extended to have more than two inputs.
- A gate can be extended to have multiple inputs if the binary operation it represents is commutative and associative.
- The AND and OR operations defined in Boolean algebra have these two properties.
- For the OR function, we have

$$x + y = y + x \quad \text{commutative}$$


and

$$(x + y) + z = x + (y + z) = x + y + z \quad \text{associative}$$

- The NAND and NOR functions are commutative and other gates can be extended to have more than two inputs, with slight definition change.
- NOR (or NAND) gate can be defined as complemented OR (or AND) gate.
- Thus, by definition, we have
$$x \downarrow y \downarrow z = (x + y + z)'$$
$$x \uparrow y \uparrow z = (xyz)'$$

The graphic symbols for the 3-input gates are shown in Fig .2-7.


.

 

(a) Three-input NOR gate



(b) Three-input NAND gate

 

(c) Cascaded NAND gates


FIGURE 2-7

Multiple-input and cascaded NOR and NAND gates


- In writing cascaded NOR and NAND operations, one must use the correct parentheses to signify proper sequence of gates.
- For example, consider the circuit of Fig 2-7 (c)
- The Boolean function for the circuit must be written as

$$F = [(ABC)'(DE)']' = ABC + DE$$
- The second expression is obtained from DeMorgan's theorem.
- It also shows that an expression in sum of products can be implemented with NAND gates.
- The exclusive-OR and equivalence gates are both commutative and associative and can be extended to more than two inputs.
- The exclusive-OR is an odd function, i.e., it is equal to 1 if an odd number of input variables are equal to 1.

 - The construction of a 3-input exclusive-OR function is shown in (a).



(a) Using 2-input gates

 

(b) 3-input gate

<i>x</i>	<i>y</i>	<i>z</i>	<i>F</i>
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(c) Truth table

FIGURE 2-8
3-input exclusive-OR gate

- It is normally implemented by cascading 2-input gates, as shown in (a).
- Graphically, it can be represented with a single 3-input gate.
- Notice that for three input exclusive-OR gate(s), the output is 1 when an odd number of inputs, 1 or 3 in this case, are 1.

2-8 INTEGRATED CIRCUITS

- Digital circuits are constructed with integrated circuits.
- An integrated circuit (IC) is a small silicon semiconductor crystal, called a chip, containing the electronic components for the digital gates.
- The various gates are interconnected inside the chip to form the required circuit.
- The chip is mounted in a ceramic or plastic container, and connections are welded to external pins to form the integrated circuit.
- The number of pins may range from 14 in a small IC package to 64 or more in a larger package.
- The size of the IC package is very small.
- For example, an entire microprocessor is enclosed within a 64-pin package with dimensions of 50 X15X4 millimeters.

- Each IC has a numeric designation printed on the surface of the package for identification.
- Vendors publish data books that contain descriptions and other information about the IC's that they manufacture.

Levels of Integration

- Digital ICs are often categorized according to their circuit complexity as measured by the number of logic gates in a single package.
- They are categorized as small scale, medium scale, and large scale integration devices depending on the number of internal gates they have.
- **Small-scale integration (SSI)** devices contain several independent gates in a single package.
- The inputs and outputs of the gates are connected directly to the pins in the package.
- The number of gates is usually fewer than 10 and is limited by the number of pins available in the IC.
- **Medium-scale integration (MSI)** have approximately 10 to 100 gates in a single package and are used to build decoders, adders or multiplexers.

- **Large-scale integration (LSI)** devices contain between 100 and a few thousands gates in a single package.
- They include digital systems as processors, memory chips, and programmable logic devices.
- **Very large-scale integration (VLSI)** devices contain thousands of gates within a single package.
- Examples are large memory arrays and complex microcomputer chips.

Digital Logic Families

- Digital integrated circuits are classified by not only their complexity or logical operation, but also by the specific circuit technology to which they belong.
- The circuit technology is referred to as digital logic family.

- Each logic family has its own basic electronic circuit upon which more complex digital circuits and components are developed.
- The basic circuit in each technology is a NAND, NOR, or an inverter gate.
- The electronic components used in the construction of the basic circuit are usually used as the name of the technology.
- Many different logic family of integrated circuits have been introduced commercially.
- The following are the most popular
 - TTL transistor-transistor logic
 - ECL emitter-coupled logic
 - MOS metal-oxide semiconductor
 - CMOS complementary metal-oxide semiconductor

- TTL is a widespread logic family that has been in operation for some time and is considered as standard.
- ECL has an advantage in systems requiring high-speed operation.
- MOS is suitable for circuits that need high component density, and CMOS is preferable in systems requiring low power consumption.,
- The transistor-transistor logic family evolved from a previous technology that used diodes and transistors for the basic NAND gate.
- This technology was called DTL for diode-transistor logic.
- Later the diodes were replaced by transistors to improve the circuit operation.
- The name of the logic family was changed to TTL as a result.


- Emitter-coupled logic (ECL) circuits provide the highest speed among the integrated digital logic families.
- ECL is used in systems such as supercomputers and signal processors, where high speed is essential.
- The transistors in ECL gates operate in a non-saturated state, a condition that allows the achievement of propagation delays of 1 to 2 nanoseconds.
- The metal-oxide semiconductor (MOS) is a unipolar transistor that depends upon the flow of only one type of carrier, which may be electrons (n-channel) or hole (p-channel).
- This is in contrast to the bipolar transistor used in TTL and ECL gates, where both carriers exist during normal operation.
- A p-channel MOS is referred to as PMOS and n-channel as NMOS

- NMOS is the one that is currently used in circuits with only one type of MOS transistor.
- Complementary MOS (CMOS) technology uses one PMOS and one NMOS transistor connected in a complementary fashion in all circuits.
- The most important advantages of MOS over bipolar transistors are the high packing density of circuits, and a simpler processing technique during fabrication.
- Also MOS technology encompasses a more economical operation because of the low-power consumption.
- The characteristics of digital logic families are usually compared by analyzing the circuit of the basic gate in each family.
- The most important parameters that are evaluated and compared are as follows:


- *Fan-out* specifies the number of standard loads that the output of a typical gate can drive without impairing its normal operation.
- A standard load is usually defined as the amount of current needed by an input of another similar gate of the same family.
- *Power dissipation* is the power consumed by the gate that must be available from the power supply.
- *Propagation delay* is the average transition delay time for the signal to propagate from input to output.
- The operating speed is inversely proportional to the propagation delay.
- *Noise Margin* is the minimum external noise voltage that causes an undesirable change in the circuit output.

Integrated Circuits

 - Some typical SSI circuit are shown in Fig 2-9.
- Each IC is enclosed within a 14 or 16-pin package.
- A notch placed on the left side of the package is used to reference the pin numbers.
- The pins are numbered along two sides starting from the notch and continuing counterclockwise.
- The inputs and outputs of the gates are connected to the package pins, as indicated in each diagram.




7404—Hex inverters

 


7400—Quadruple 2-input NAND gates

(a) TTL gates.

 


10102—Quadruple 2-input NOR gates

 


10107—Triple exclusive-OR/NOR gates

(b) ECL gates.

 

4002—Dual 4-input NOR gates.

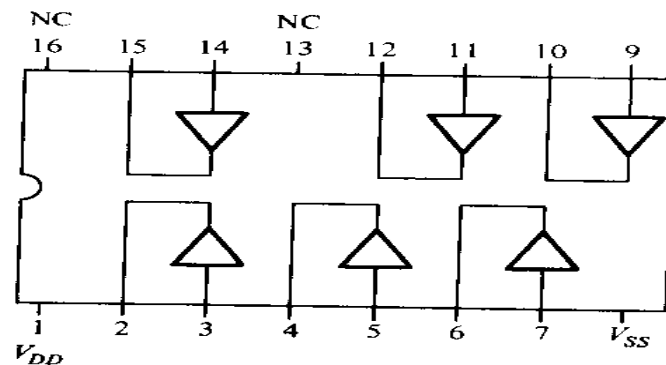

4050—Hex buffers.

(c) CMOS gates.

FIGURE 2-9

Some typical integrated-circuit gates

- TTL IC's are usually distinguished by their numerical designation as the 5400 and 7400 series.
- The former has a wide operating temperature range, suitable for military use.
- And the latter has a narrower temperature range, suitable for commercial use.
- The numerical designation of 7400 series means that IC packages are numbered as 7400, 7401, 7402, etc.
- Fig 2-9(a) shows two TTL SSI circuits.
- The 7404 provides six (hex) inverters in a package.
- The 7400 provides four (quadruple) 2-input NAND gates
- The terminal marked V_{cc} and GRD (ground) are the power supply pins that require a voltage of 5 volts for proper operation.

- The two logic levels for TTL are 0 and 3.5 volts.
- The TTL logic family actually consists of several subfamilies or series.
- Table 2-9 lists the name of each series and the prefix designation that

TABLE 2-9
Various Series of the TTL Logic Family

TTL Series	Prefix	Example
Standard TTL	74	7486
High-speed TTL	74H	74H86
Low-power TTL	74L	74L86
Schottky TTL	74S	74S86
Low-power Schottky TTL	74LS	74LS86
Advanced Schottky TTL	74AS	74AS86
Advanced Low-power Schottky TTL	74ALS	74ALS86

- The differences between the various TTL series are in their electrical characteristic, such as power dissipation, propagation delay, and switching speed.
- They do not differ in the pin assignment or logic operation performed by the internal circuits.
- The most common ECL ICs are designated as 10000 series.
- Fig 2-9(b) shows two ECL circuits.
- The 10102 provides four 2-input NOR gates.
- Note that an ECL gate may have two outputs, one for the NOR function and another for the OR function.
- The 10107 IC provides three exclusive-OR gates.

- ECL gates have three terminals for power supply.
- V_{CC1} and V_{CC2} are usually connected to ground, and V_{EE} to a -5.2 volt supply.
- The two logic level for ECL are -0.8 and -1.8
- CMOS circuits of the 4000 series are shown in Fig 2-9(c).
- Only two 4-input NOR gates can be accommodated in the 4002 because of pin limitation.
- The 4050 IC provides six buffer gates.
- Both ICs have unused terminals marked NC (no connection).
- The terminals marked V_{DD} requires a power-supply voltage from 3 to 15 volts.

- V_{ss} is usually connected to ground.
- The two logic levels are 0 and V_{DD} volts.
- The original 4000 series of CMOS circuits was designed independently from the TTL series.
- Since TTL became a standard in the industry, vendors started to supply other CMOS circuits that are pin compatible with similar TTL ICs.
- The CMOS series available commercially are listed in Table 2-10.
- The 74H series operates at higher speeds than the 74 C series.
- The 74HCT series is both electrically and pin compatible with TTL devices.
- This means that 74HCT ICs can be connected directly to TTL ICs without interfacing.

TABLE 2-10
Various Series of the CMOS Logic Family

CMOS series	Prefix	Example
Original CMOS	40	4009
Pin compatible with TTL	74C	74C04
High-speed and pin compatible with TTL	74HC	74HCO4
High-speed and electrically compatible with TTL	74HCT	74HCT04