
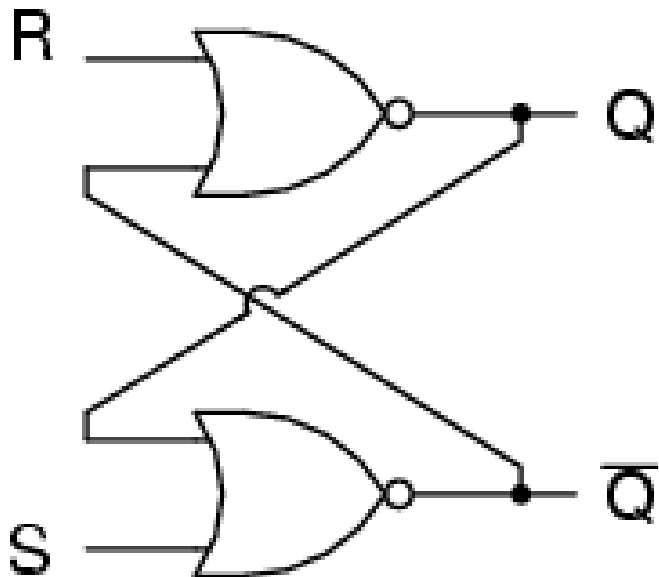


# SR NOR LATCH

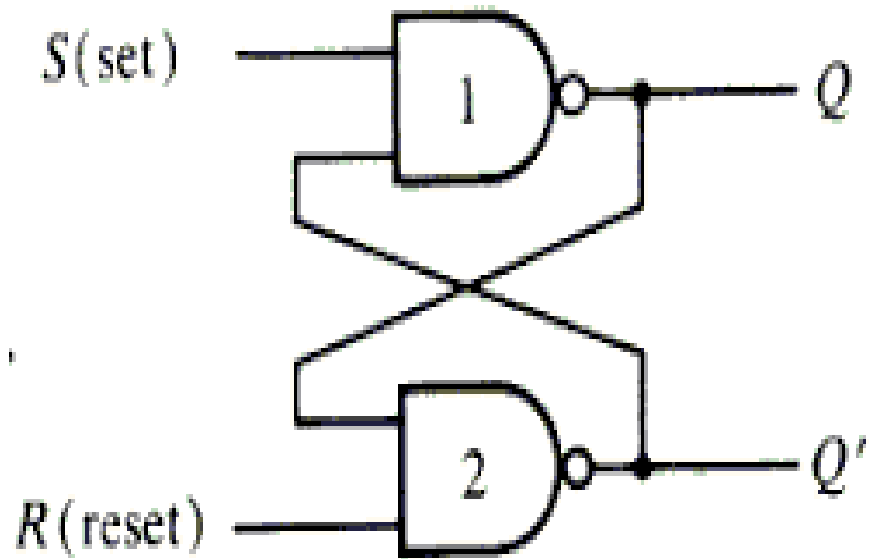

S	R	Q	$\bar{Q}$
0	0	latch	latch
0	1	0	1
1	0	1	0
1	1	0	0

# SR NAND LATCH




(a) Logic diagram


$S$	$R$	$Q$	$Q'$	
1	0	0	1	
1	1	0	1	(after $S = 1, R = 0$ )
0	1	1	0	
1	1	1	0	(after $S = 0, R = 1$ )
0	0	1	1	

(b) Truth table

# SR FF

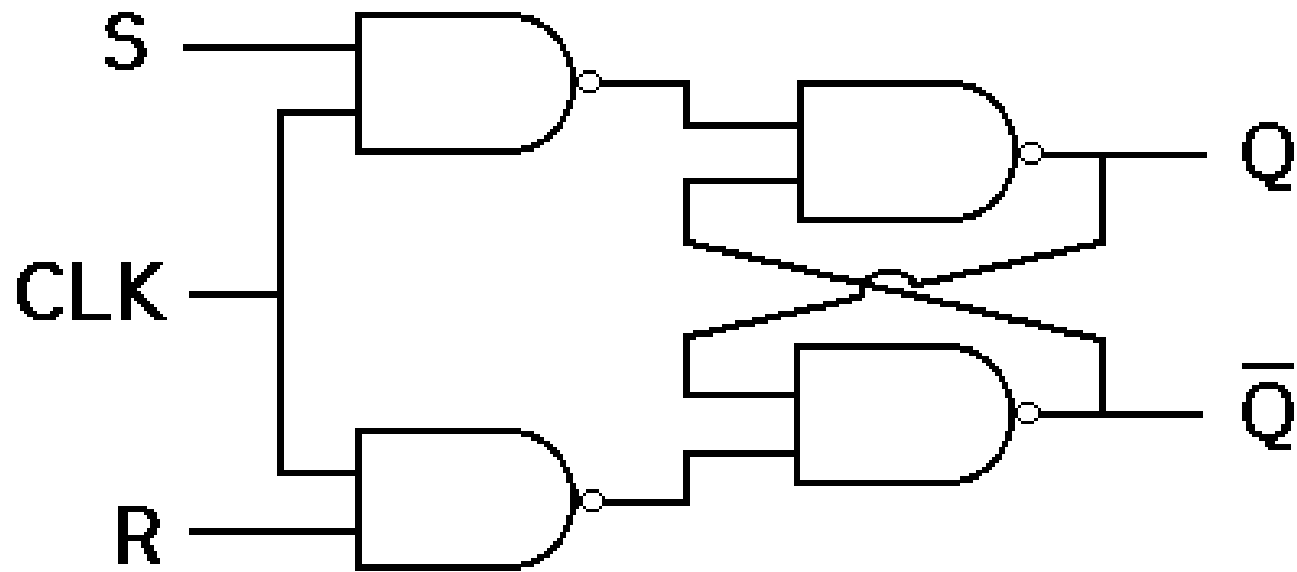


# D FF

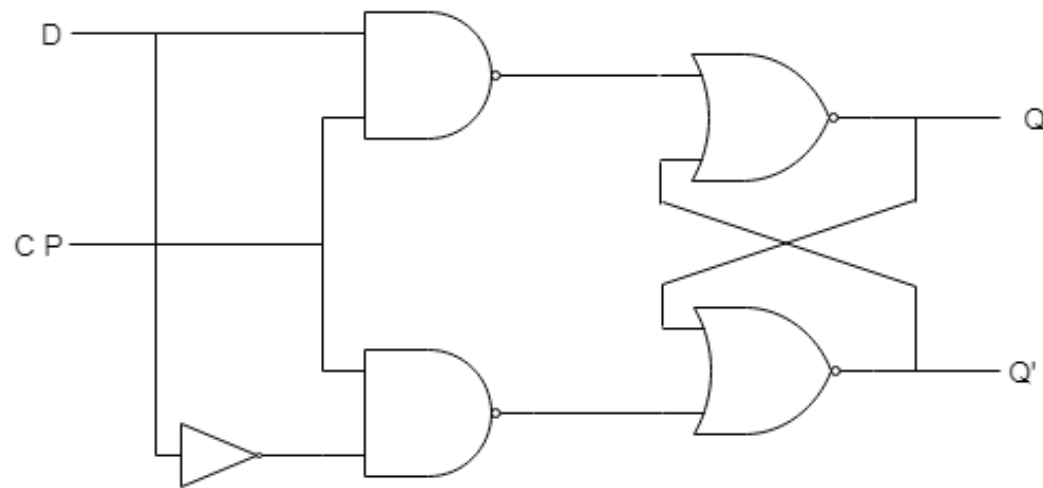

(a) Logic diagram with Nand gates

Q	D	Q (t+1)
0	0	0
0	1	1
1	0	0
1	1	1


(c) Transition table

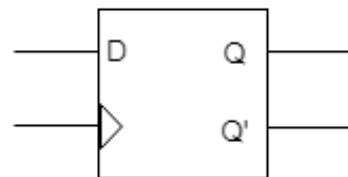


(b) Graphic Symbol

fig. Clocked D flip flop


# JK FF

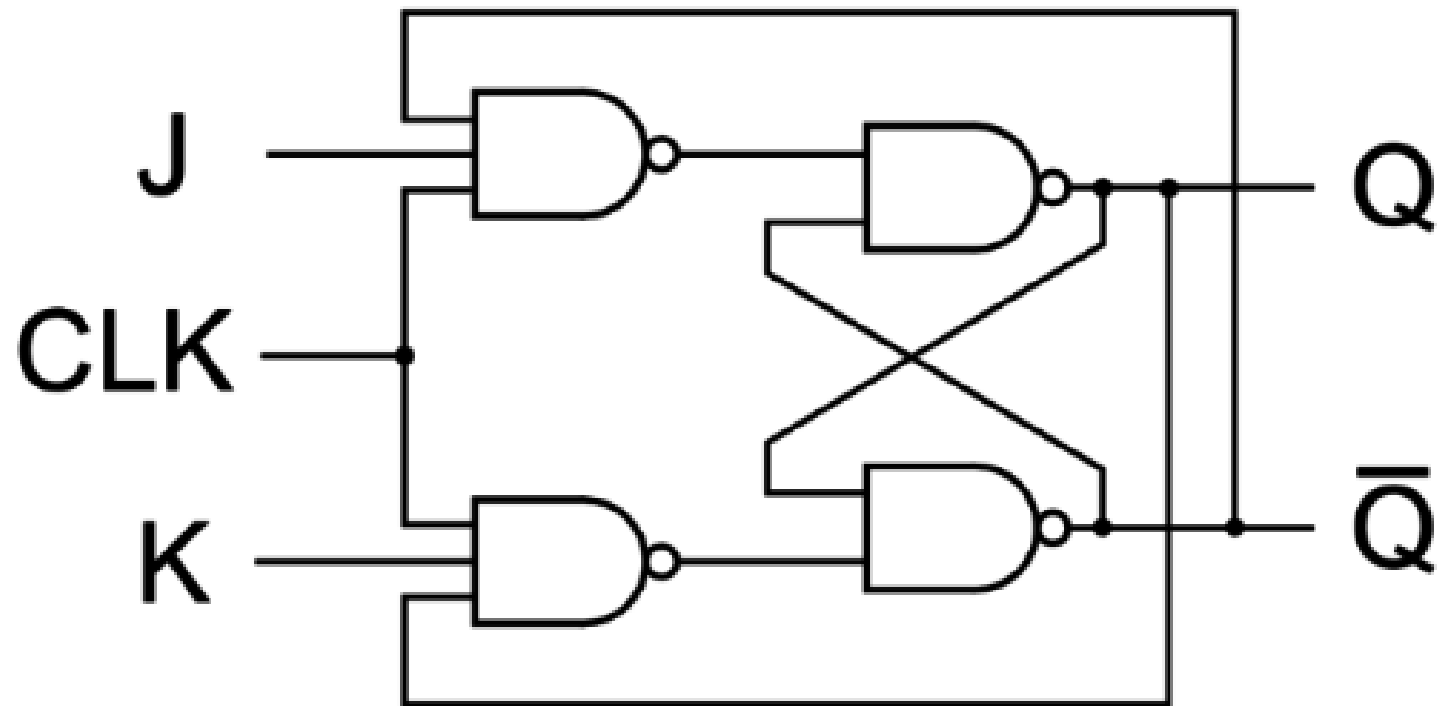


# Racing in JK FF

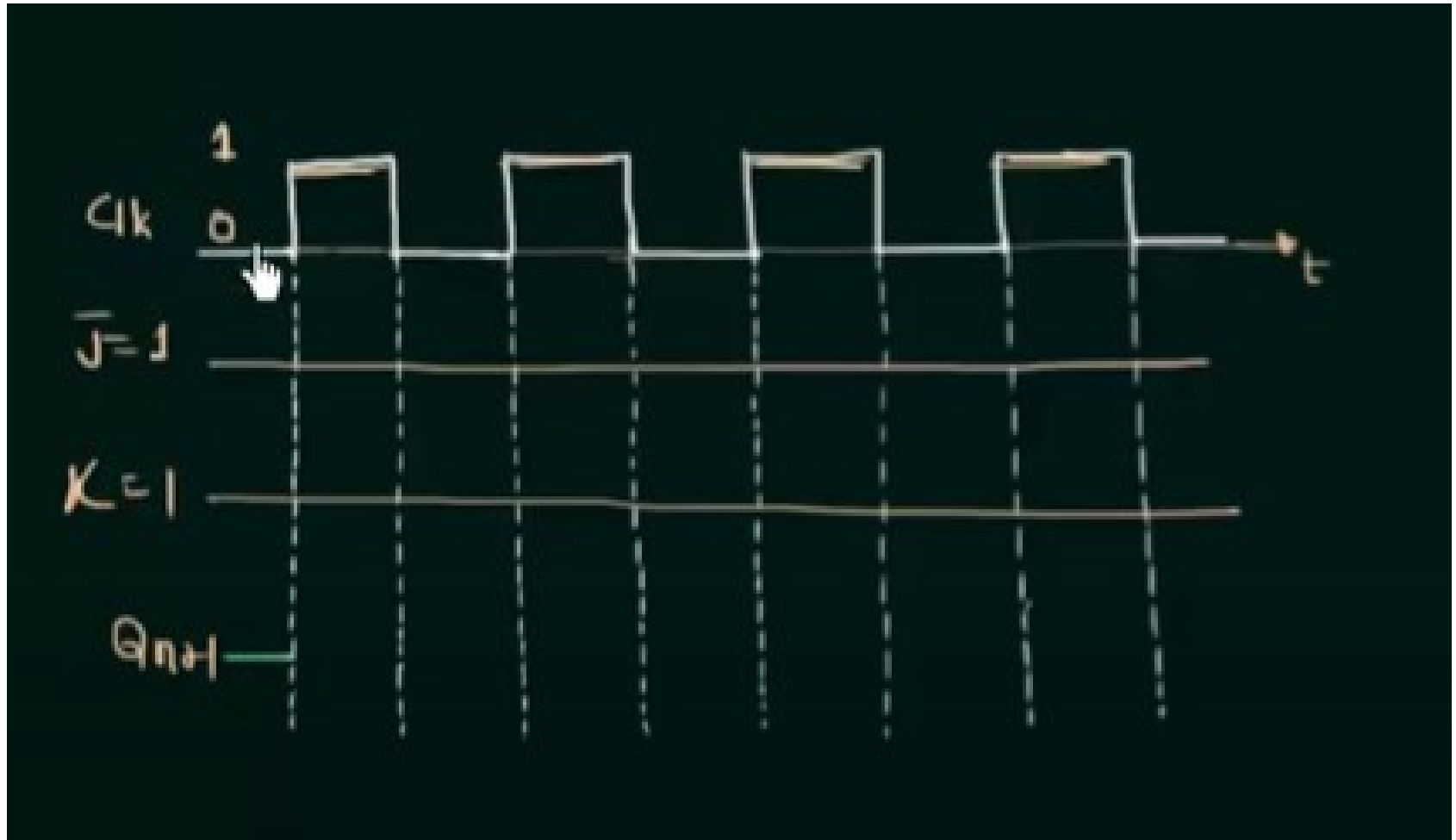

# Race Around Condition - JK FF

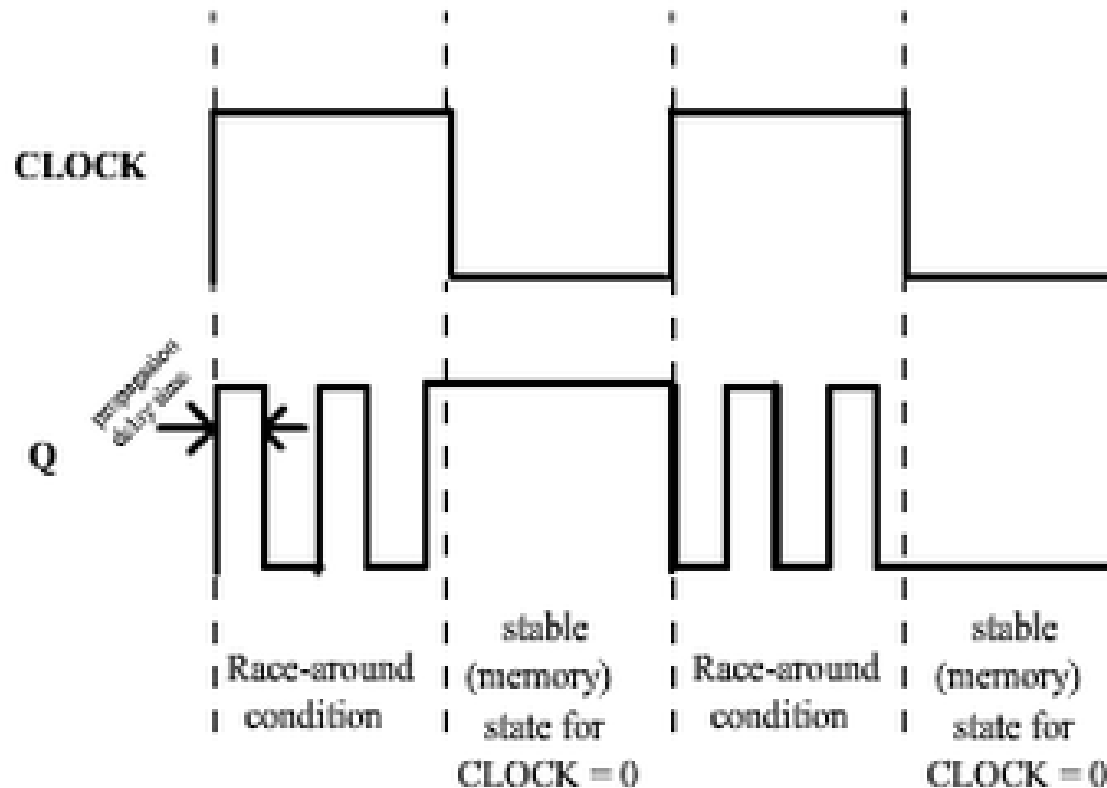

# Master Slave JK FF

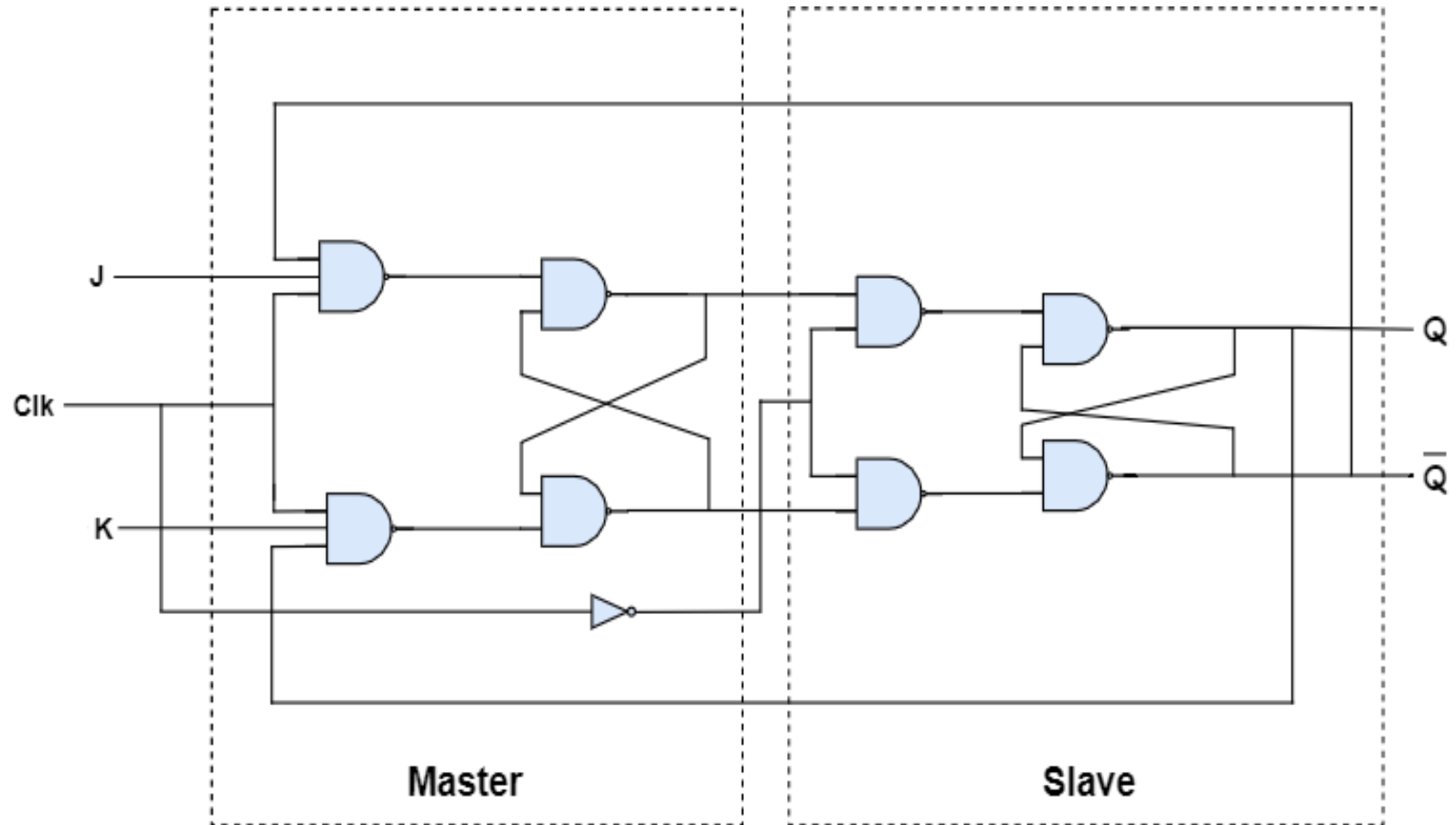





# Master Slave JK FF



# Master Slave D FF

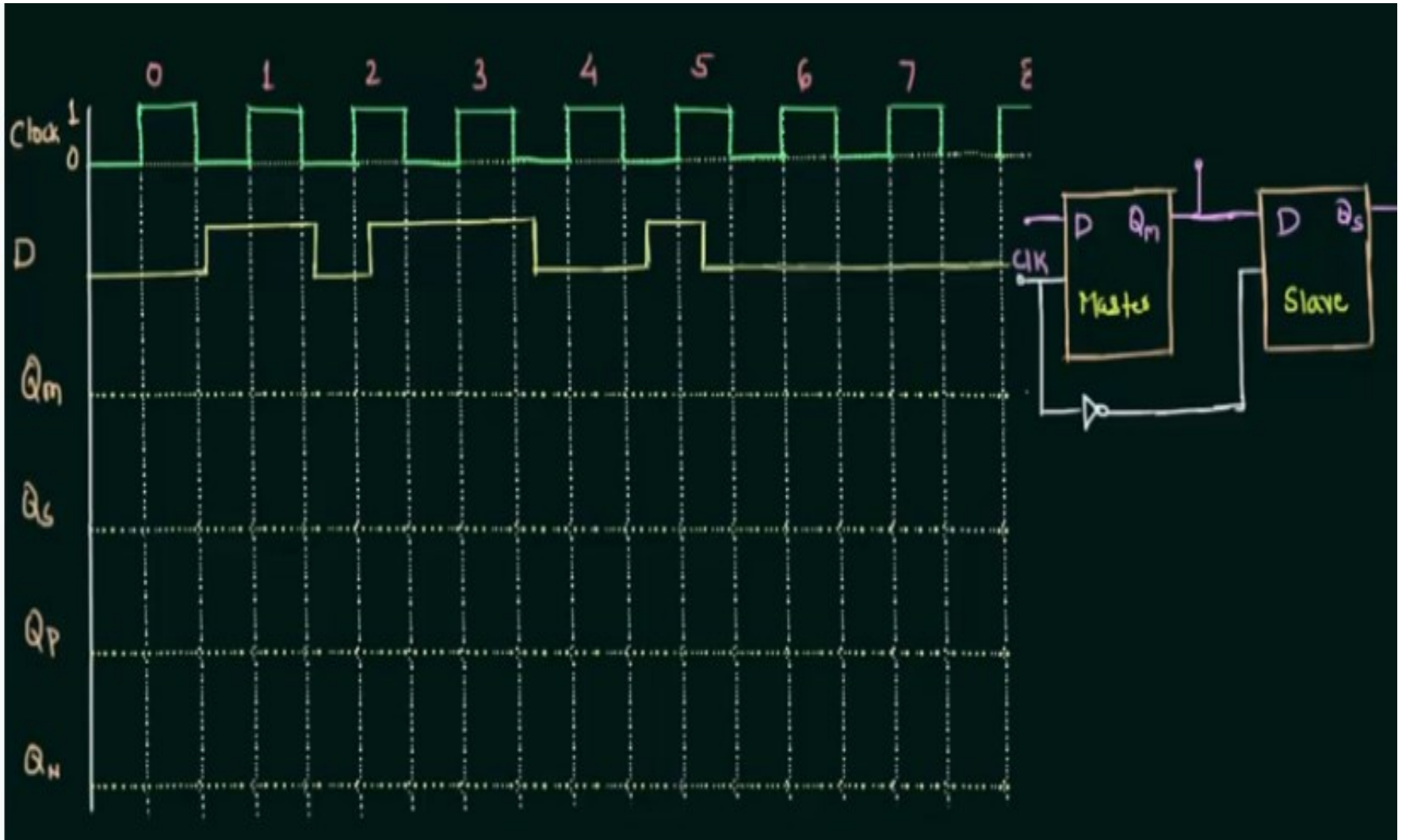

# T FF

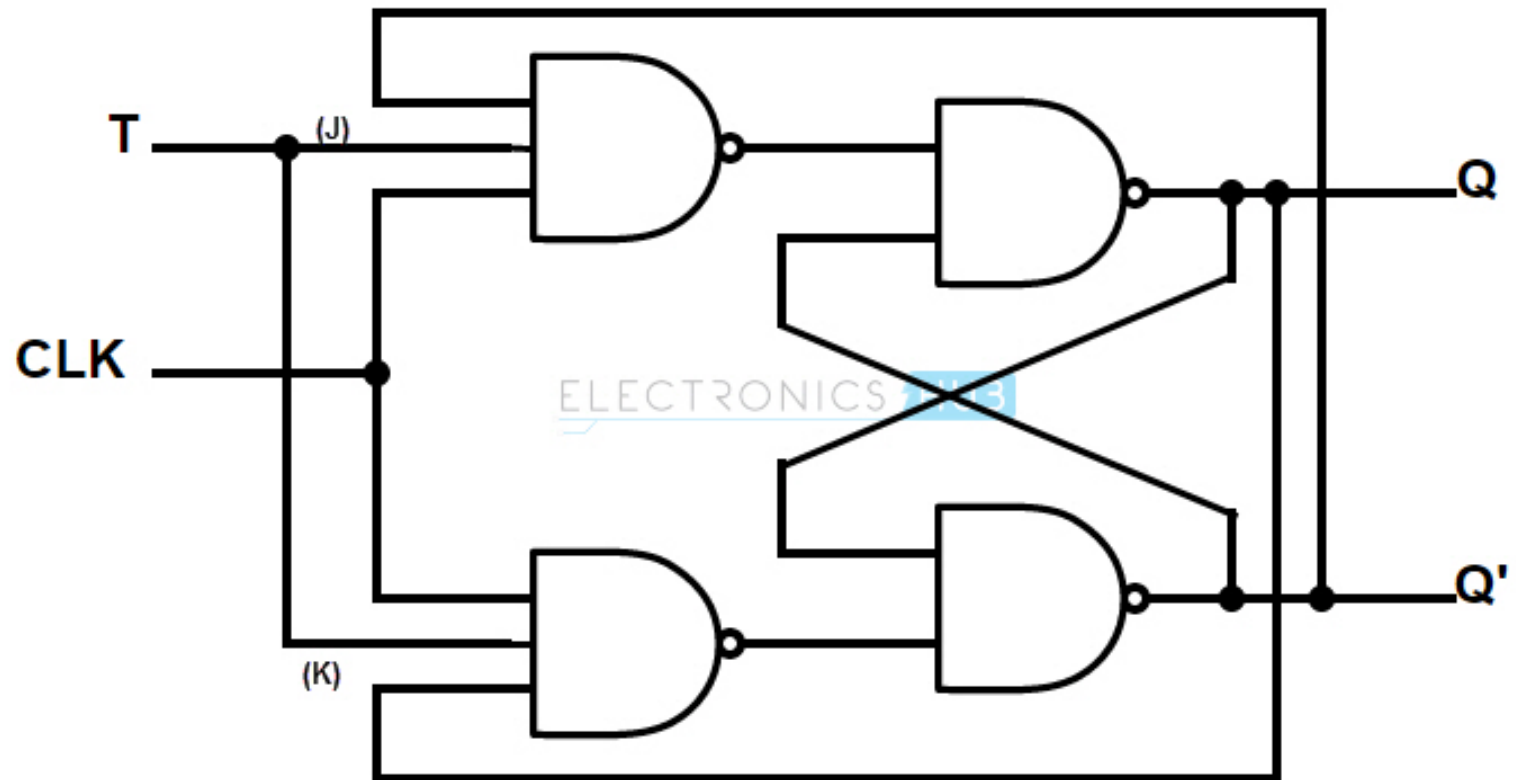

# Steps for FF Conversion

- Identify available and required flip flop
- Make characteristic table for required flip flop
- Make excitation table for available flip flop
- Write Boolean expression for available flip flop
- Draw the circuit

E.g. JK to D, T to D, SR to JK, SR to T, JK to SR and T to SR.....

# SR FF Truth, X/c and Excitation Table

Clk	S	R	Q <sub>n+1</sub>
0	X	X	Q <sub>n</sub>
1	0	0	Q <sub>n</sub>
1	0	1	0
1	1	0	1
1	1	1	Invalid

Q <sub>n</sub>	Q <sub>n+1</sub>	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

Q <sub>n</sub>	S	R	Q <sub>n+1</sub>
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	X
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	X

# D FF Truth, X/c and Excitation Table

Clk	D	Q <sub>n+1</sub>
0	X	Q <sub>n</sub>
1	0	0
1	1	1

Q <sub>n</sub>	D	Q <sub>n+1</sub>
0	0	0
0	1	1
1	0	0
1	1	1

Q <sub>n</sub>	Q <sub>n+1</sub>	D
0	0	0
0	1	1
1	0	0
1	1	1

# JK FF Truth, X/c and Excitation Table

Clk	J	K	Q <sub>n+1</sub>
0	X	X	Q <sub>n</sub>
1	0	0	Q <sub>n</sub>
1	0	1	0
1	1	0	1
1	1	1	Q <sub>n</sub> '

Q <sub>n</sub>	Q <sub>n+1</sub>	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Q <sub>n</sub>	J	K	Q <sub>n+1</sub>
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

# T FF Truth, X/c and Excitation Table

Clk	T	Q <sub>n+1</sub>
0	X	Q <sub>n</sub>
1	0	Q <sub>n</sub>
1	1	Q <sub>n</sub> '

Q <sub>n</sub>	T	Q <sub>n+1</sub>
0	0	0
0	1	1
1	0	1
1	1	0

Q <sub>n</sub>	Q <sub>n+1</sub>	T
0	0	0
0	1	1
1	0	1
1	1	0