

Chapter 3 : Simplification of Boolean Functions

3-1 The Map Method

3-2 Two- and Three-Variable Maps

3-3 Four Variable Map

3-4 Five Variable Map

3-5 Product of Sums Simplification

3-6 NAND and NOR Implementation

3-7 Other Two- Level Implementations

3-8 Don't Care Conditions

- **3-9 The Tabulation Method**
- **3-10 Determination of Prime Implicants**
- **3-11 Selection of Prime Implicants**


3-1 THE MAP METHOD

- One can simplify Boolean function using boolean algebra.
- However, this procedure of minimization is awkward because it lacks specific rules to predict each succeeding step in the manipulative process.
- The map method provides a simple straightforward procedure for minimizing Boolean functions.
- This method may be regarded either as a pictorial form of a truth table or as an extension of the Venn diagram.
- The map method, first proposed by Veitch and modified by Karnaugh, is also known as the “Veitch diagram” or the “Karnaugh map.”
- The map is a diagram of squares.
- Each square represents a minterm.


- It is known that any Boolean function can be expressed as sum of minterms.
- Hence, a Boolean function is recognized graphically in the map from the area enclosed by those squares whose minterms are included in the function.
- In fact, the map presents a visual diagram of all possible ways a function may be expressed in standard form.
- By recognizing various patterns, the user can derive alternative algebraic expressions for the same function, from which he can select the simplest one.
- We shall assume that the simplest algebraic expression is any one in a sum of products or products of sums that has a minimum number of literals.

 3-2 TWO- AND THREE-VARIABLE MAPS

A two variable map is shown in Fig 3-1(a)



(a)

 

(b)

FIGURE 3-1

Two-variable map

- There are four minterms for two variables.
- Therefore, the map consists of four squares, one for each minterm.
- The map is redrawn in (b) to show the relationship between the squares and the two variables.

- The 0's and 1's marked for each row and each column designate the values of the variables x and y , respectively.
- Notice that x appears primed in row 0 and unprimed in row 1.
- Similarly, y appears primed in column 0 and unprimed in column 1.
- Let us we mark the squares whose minterms belong to a given function.
- Then, the two-variable map become another useful way to represent any one of the 16 Boolean functions of two variables.

 


FIGURE 3-2

Representation of functions in the map

As an example, the function xy is shown in Fig 3-2(a).

Since xy is equal to m_3 , a 1 is placed inside the square that belongs to m_3 .

Similarly, the function $x + y$ is represented in the map of Fig 3-2 (b) by three squares marked with 1's.

- These squares are found from the minterms of the function:
 - $x + y = x'y + xy' + xy = m_1 + m_2 + m_3$
- A three variable map is shown in Fig 3-3.

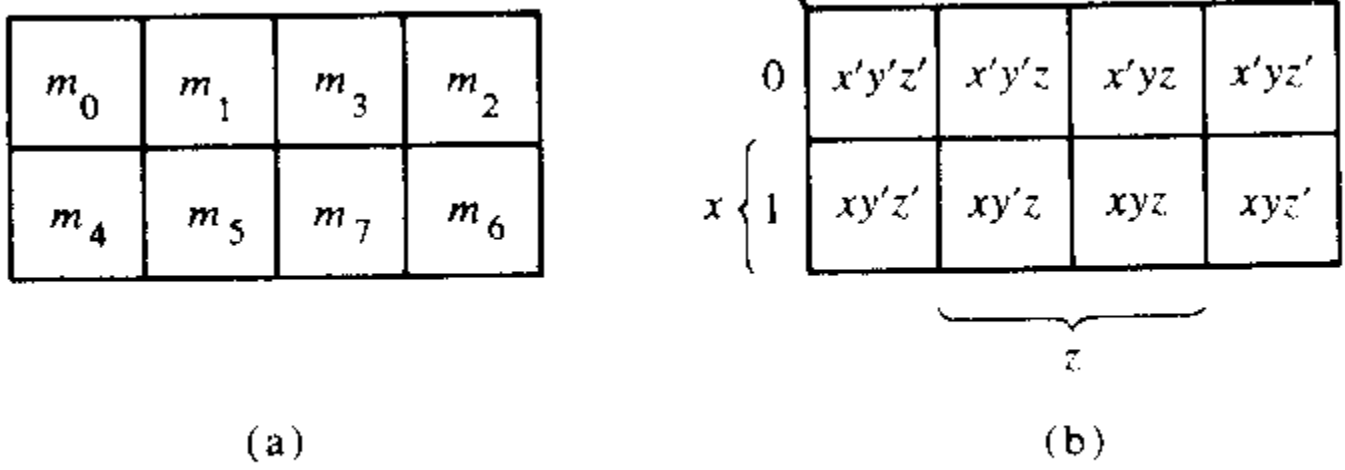


FIGURE 3-3
Three-variable map

- There are eight minterms for three binary variables.
- Therefore, a map consists of eight squares.
- Note that the minterms are not arranged in a binary sequence, but in a sequence similar to the Gray code.
- Only one bit changes from 1 to 0 or from 0 to 1 as we move to adjacent square.
- The map drawn in part(b) is marked with numbers in each row and column to show the relationship between the squares and the three variables.
- For example, the square assigned to m_5 corresponds to row 1 and column 101.
- When these two numbers are read as 101, they give the decimal number 5, hence minterm 5(m_5).

- square $m_5 = xy'z$ can be considered to be in the row marked x and the column belonging to $y'z$ (column 01).
- Note that there are four squares where each variable is equal to 1 and four where each is equal to 0.
- The variable appears unprimed in those four squares where it is equal to 1 and primed in those squares where it is equal to 0.
- To understand the usefulness of the map for simplifying Boolean functions, we must be aware of the basic property possessed by adjacent squares.
- Any two adjacent squares in the map differ by only one variable, which is primed in one square and unprimed in the other.
- For example, m_5 and m_7 , lie in two adjacent squares.

- Variable y is primed in m_5 and unprimed in m_7 .
- The other two variables are the same in both squares.
- From the postulates of Boolean Algebra,
 - $m_5 + m_7 = xy'z + xyz = xz(y + y') = xz$
- Variable y can be removed when the where the two minterms are ORed.
- Thus, any two minterms in adjacent squares that are ORed together will cause the removal of the different variable.
- **Example 3-1**
- Simplify the Boolean function
 - $F(x, y, z) = \sum(2, 3, 4, 5)$

- First, a 1 is marked in each minterm that represents the function.
- This is shown in Fig 3-4.
- The squares for minterms 010, 011, 100, and 101 are marked with 1's.

		yz		y	
x		00	01	11	10
x	0			1	1
	1	1	1		

z

FIGURE 3-4

Map for Example 3-1; $F(x, y, z) = \Sigma (2, 3, 4, 5) = x'y + xy'$

- The next step is to find possible adjacent squares.
- These are indicated in the map by two rectangles, each enclosing two 1's.
- The upper right rectangle represents the area enclosed by $x'y$.
- This is determined by observing that the two-area is in row 0, corresponding to x' .
- And the last two column correspond to y .
- Similarly, the lower left rectangle represents the product term xy' .
- The second row represents x .
- And the two left columns represent y' .

- The logical sum of these two product terms gives the simplified expression:

$$•F = x'y + xy'$$

- There are cases where the two squares in the map are considered to be adjacent even though they do not touch each other.
- In Fig 2-3, m_0 is adjacent to m_2 and m_4 is adjacent to m_6 .
- The reason is that the minterms differ by one variable.
- Consequently, we must modify the definition of adjacent squares to include this and other similar cases.
- This is done by considering the map as being drawn on a surface where the right and left edges touch each other to form adjacent squares.

- **Example 3-2**
- Simplify the Boolean function
 - $F(x, y, z) = \sum(3, 4, 6, 7)$
- The map for this function is shown in Fig 3-5.

		yz			
		00	01	11	10
x	0			1	
	1	1		1	1

FIGURE 3-5

Map for Example 3-2; $F(x, y, z)$
 $\sum(3, 4, 6, 7) = yz + xz'$

- There are four squares marked with 1's, one for each minterm.
- Two adjacent squares are combined in the third column to give yz .
- The remaining two squares with 1's are also adjacent by the new definition.
- They are shown in the diagram with their values enclosed in half rectangles.
- These two squares when combined give the term xz' .
- The simplified function becomes

$$F = yz + xz'$$

- Consider now any combination of four adjacent squares in the three- variable map.
- Any such combination represents the logic sum of four minterms.
- And it results in an expression of only one literal.
- For example, the logic sum of four adjacent minterms 0, 2, 4, and 6 reduces to a single literal term z' .
- $$\begin{aligned} m_1 + m_2 + m_4 + m_6 &= x'y'z + x'yz' + xy'z' + xyz' \\ &= x'z'(y + y') + xz'(y + y') \\ &= x'z' + xz' \\ &= z'(x + x') = z' \end{aligned}$$
- The number of adjacent squares that may be combined must always represent a number that is a power of two such as 1, 2, 4, and 8.

- As a larger number of adjacent squares are combined, we obtain a product term with fewer literals.
- One square represents one minterm, giving a term of three literals.
- Two adjacent squares represent a term of two literals.
- Four adjacent squares represent a term of one literal.
- Eight adjacent squares encompass the entire map and produce a function that is always equal to 1.

•Example 3-3

•Simplify the Boolean function

$$F(x, y, z) = \sum(0, 2, 4, 5, 6)$$

•The map for F is shown in Fig 3-6.

 


FIGURE 3-6

Map for Example 3-3; $F(x, y, z) = \sum(0, 2, 4, 5, 6) = z' + xy'$

- First, we combine the four adjacent squares in the first and last columns to give the single literal term z' .
- The remaining single square representing the minterm 5 is combined with an adjacent square that has already been used once.
- This is permitted and is necessary since the two adjacent squares give the two literal term xy' .
- The simplified function is:

$$F = z' + xy'$$

- If a function is not expressed in sum of minterms, it is possible to use the map to obtain the minterms of the function.
- And then we can simplify the function to an expression with a minimum number of terms.

- It is necessary to make sure that the algebraic expression is in sum of products form.
- Each product term can be plotted in the map in one, two, or more squares.
- The minterms of the function are then read directly from the map.
- **Example 3-4**
- Given the following Boolean function:
 - $F = A'C + A'B + AB'C + BC$
- (a) Express it in sum of minterms
- (b) Find the minimal sum of products expression
- Three product terms in the expression have two literals and are represented in a three variable map by two squares each.

 


FIGURE 3-7

Map for Example 3-4; $A'C + A'B + AB'C + BC = C + A'B$

- The two squares corresponding to the first term $A'C$ are found in Fig 3-7.
- The coincidence of A' (first row) and C (two middle columns) to give squares 001 and 011.

- Note that when marking 1's in the squares, it is possible to a 1 already placed there from a preceding term.
- This happens with the second term $A'B$, which has 1's in squares 011 and 010.
- But square 011 is common with the first term $A'C$, so only one 1 is marked in it.
- Continuing in this fashion, we determine that the term $AB'C$ belongs in square 101, corresponding to minterm 5.
- And the tem BC has two 1's in squares 011 and 111.
- The function has a total of five minterms, as indicated by the five 1's in the map of Fig 3-7.
- The minterms are read directly from the mp to be 1, 2, 3, 5, 7

- The function can be expressed in sum of minterms form:

- $F(A, B, C) = \sum(1, 2, 3, 5, 7)$

- The simplified form results in the following expression:

- $F = C + A'B$

- Exercises**

- Simplify the following function using three variable maps:**

- (a) $F(x, y, z) = \sum(3, 5, 6, 7)$**

- (b) $F(x, y, z) = \sum(0, 2, 3, 4, 6)$**

3-3 Four Variable Map

- The map for Boolean function of four binary variables is shown in Fig 3-8.
- In (a) are listed the 16 minterms and the squares assigned to each.
- In (b) the map is redrawn to show the relationship with four variables.

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6
m_{12}	m_{13}	m_{15}	m_{14}
m_8	m_9	m_{11}	m_{10}

(a)

		y			
		yz	01	11	10
w	x	00	01	11	10
	00	$w'x'y'z'$	$w'x'y'z$	$w'x'yz$	$w'x'yz'$
	01	$w'xy'z'$	$w'xy'z$	$w'xyz$	$w'xyz'$
	11	$wxy'z'$	$wxy'z$	$wxyz$	$wxyz'$
	10	$wx'y'z'$	$wx'y'z$	$wx'yz$	$wx'yz'$

z

(b)

FIGURE 3-8

Four-variable map

- The rows and column are numbered in a reflected-code sequence, with only one digit changing value between two adjacent rows and column.
- The minterm corresponding to each square can be obtained from the concatenation of the row number with the column number.
- For example, the numbers of the third row (11) and the second column (01), when combined give the binary number 1101, equivalent to 13.
- Thus, the square in the third row and the second column represent the minterm m_{13} .
- The map minimization is similar as before where adjacent squares are defined to be squares next to each other.
- The map is considered to lie on a surface with the top and bottom edges, as well as the right and left edges, touching each other to form adjacent squares.

- For example, m_0 and m_2 form adjacent squares, as do m_3 and m_{11} .
- One square represent one minterm, giving a term of four literals.
- Two adjacent squares represent a term of three literals.
- Four adjacent squares represent a term of two literals.
- Eight adjacent squares represent a term of one literal.
- Sixteen adjacent squares represent the function equal to 1.
- No other combination of squares can simplify the function.
- The following two examples show the procedure used to simplify four-variable Boolean functions.

•Example 3-5

•Simplify the Boolean function

$$•F(w, x, y, z) = \sum(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$$

- Since the function has four variables, a four-variable map must be used.
- The minterms listed in the sum are marked by 1's in the map of Fig. 3-9.
- Eight adjacent squares marked with 1's can be combined to form the one literal term y' .
- The remaining three 1's on the right cannot be combined to give a simplified term.
- They must be combined as two or four adjacent squares.

 


FIGURE 3-9

Map for Example 3-5; $F(w, x, y, z) = \Sigma(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14) = y' + w'z' + xz'$

- The larger the number of squares combined, the smaller the number of literals in the term.
- In this example, the top two 1's on the right are combined with the top two 1's on the left to give the term $w'z'$.
- Note that it is permissible to use the same square more than once.
- We are now left with a square marked by 1 in the third row and fourth column (square 1110).
- Instead of taking this square alone (which will give a term of four literals), we combine it with squares already used to form an area of four adjacent squares.
- These squares comprise the two middle rows and the two end columns.
- They give the term xz' .

- The simplified function is

$$•F = y' + w'z' + xz'$$

•**Example 3-6**

- Simplify the Boolean function

$$•F = A'B'C' + B'CD' + A'BCD' + AB'C'$$

- The area of the map covered by this function consists of the squares marked with 1's in Fig 3-10.
- This function has four variables, and as expressed, consists of three terms, each with three literals, and one term of four literals.
- Each term of three literals is represented in the map by two squares.

 


FIGURE 3-10

Map for Example 3-6; $A'B'C' + B'CD' + A'BCD' + AB'C' + B'D' + B'C' + A'CD'$


- For example, $A'B'C'$ is represented in squares 0000 and 0001.
- The function can be simplified in the map by taking the 1's in the four corners to give the term $B'D'$.
- This is possible because these four squares are adjacent when the map is drawn in a surface with top and bottom or left and right edges touching one another.
- The two left hand 1's in the top row are combined with the two 1's in the bottom to give the term $B'C'$.
- The remaining 1 may be combined in a two-square area to give the term $A'CD'$.
- The simplified function is:
 - $F = B'D' + B'C' + A'CD'$

Prime Implicants

- When choosing adjacent squares in a map, we must ensure that all the minterms of the function are covered when combining the squares.
- It is also necessary to minimize the number of terms in the expression.
- And it is important to avoid any redundant terms whose minterms are already covered by other terms.
- Sometimes there may be two or more expressions that satisfy the simplification criteria.
- The procedure for combining squares in the map may be made more systematic if we understand the meaning of the terms prime implicants.
- A **prime implicant** is a product term obtained by combining the maximum possible number of adjacent squares in the map.

- If a minterm in a square is covered by only one prime implicant, that prime implicant is said to be **essential prime implicant**.
- The prime implicants of a function can be obtained from the map by combining all possible maximum numbers of squares.
- This means that a single 1 on a map represents a prime implicant if it is not adjacent to any other 1's.
- Two adjacent 1's form a prime implicant provided they are not within a group of four adjacent squares.
- Four adjacent 1's form a prime implicant if they are not within a group of eight adjacent squares, and so on.
- The essential prime implicants are found by looking at each square marked with a 1 and checking the number of prime implicants that cover it.

- The prime implicant is essential if it is the only prime implicant that covers the minterm.
- Consider the following four-variable Boolean function:
 - $F(A, B, C, D) = \sum(0, 2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$
- The minterms of the function are marked with 1's in the maps of Fig. 3-11.
- Part(a) of the figure shows two essential prime implicants.
- One term is essential because there is only one way to include minterms m_0 within four adjacent squares.
- These four squares define the term $B'D'$.

 


(a) Essential prime implicants
 BD and $B'D'$

FIGURE 3-11

Simplification using prime implicants

 - Similarly, there is only one way that minterm m_5 can be combined with four adjacent squares and this gives the second term BD .
- The two essential prime implicants cover eight minterms.
- The remaining three minterms, m_3 , m_9 , and m_{11} , must be considered next.
- Fig 3-11(b) shows all possible ways can be covered with prime implicants.



(b) Prime implicants CD , $B'C$, AD , and AB'

FIGURE 3-11

Simplification using prime implicants

- Minterm m_3 can be covered with either prime implicant CD or $B'C$.
- Minterm m_9 can be covered with either AD or AB' .
- Minterm m_{11} is covered with any one of the four prime implicants.
- The simplified expression is obtained from the logical sum of the two essential prime implicants and any two of the four prime implicants.
- There are four possible ways that the function can be expressed with four product terms of two literals each:

$$\begin{aligned}
 \bullet F &= BD + B'D' + CD + AD \\
 &= BD + B'D' + CD + AB' \\
 &= BD + B'D' + B'C + AD \\
 &= BD + B'D' + B'C + AB'
 \end{aligned}$$

- The above example has demonstrated that the identification of the prime implicants in the map helps in determining the alternatives that are available in determining a simplified expression.
- The procedure for finding the simplified expression from the map requires that we first determine all the essential prime implicants.
- The simplified expression is obtained from the logical sum of all the essential prime implicants plus other prime implicants.
- These remaining prime implicants may be needed to cover any remaining minterms not covered by the essential prime implicants.
- Sometimes, there may be more than one way of combining squares and each combination may produce an equally simplified expression.

3-4 FIVE-VARIABLE MAP

- A five-variable map needs 32 squares and a six-variable map needs 64 squares.
- A five-variable map is shown in Fig 3-12.
- It consists of 2 four-variable maps with variables A, B, C, D, and E.
- Variable A has a different value from the first map to the second map.
- The left-hand four-variable map represents the 16 squares where $A = 0$.
- The right-hand four-variable map represents the squares where $A = 1$.

 
 


FIGURE 3-12
Five-variable map

- Minterms 0 through 15 belong with $A=0$ and minterms 16 through 31 with $A=1$.
- Each four-variable map retains the previously defined adjacency when taken separately.
- In addition, each square in the $A=0$ map is adjacent to the corresponding square in the $A=1$ map.
- For example, minterm 4 is adjacent to minterm 20 and minterm 15 to 31.
- The best way to visualize this new rule for adjacent squares is to consider the two half maps as being one on top of the other.
- Any two squares that fall one over the other are considered adjacent.

- By following the procedure used for the five-variable map, it is possible to construct a six-variable map with 4 four-variable maps to obtain the required 64 squares.
- Maps with six or more variables need too many squares and are impractical to use.
- From inspection, it is possible to show that 2^k (2 to the power of k) adjacent squares, for $k=0, 1, 2, \dots, n$, in an n -variable map, will represent an area that gives a term of $n-k$ literals.
- For the above statement to be realizable, n must be greater than k .
- When $n=k$, the entire area of the map is combined to give the identity function.
- Table 3-1 shows the relationship between the number of adjacent squares and the number of literals in the term.

TABLE 3-1

The Relationship Between the Number of Adjacent Squares and the Number of Literals in the Term

k	Number of adjacent squares 2^k	Number of literals in a term in an n -variable map					
		$n = 2$	$n = 3$	$n = 4$	$n = 5$	$n = 6$	$n = 7$
0	1	2	3	4	5	6	7
1	2	1	2	3	4	5	6
2	4	0	1	2	3	4	5
3	8		0	1	2	3	4
4	16			0	1	2	3
5	32				0	1	2
6	64					0	1

- Eight adjacent squares combine an area in the five-variable map to give the term of two literals.
- **Example 3-7**
- Simplify the Boolean function
 - $F(A, B, C, D, E) = \sum(0, 2, 4, 6, 9, 13, 21, 23, 25, 29, 31)$
- The five variable map for this function is shown in Fig. 3-13.

 
 


FIGURE 3-13

Map for Example 3-7; $F = A'B'E + BD'E + ACE$

- There are six minterms from 0 to 15 that belong to the part of the map with $A=0$.
- The other five minterms belong with $A=1$.
- Four adjacent squares in the $A=0$ map are combined to give three-literal term $A'B'E'$.
- Note that it is necessary to include A' with the term because all the squares are associated with $A=0$.
- The two squares in the column 01 and the last two rows are common to both parts of the map.
- Therefore, they constitute four adjacent squares and give the three-literal term $B'DE$.
- Variable A is not included here because the adjacent squares belong to both $A=0$ and $A=1$.

- The term ACE is obtained from the four adjacent squares that are entirely within A=1 map.
- The simplified function is the logical sum of the three terms:
 - $F = A'B'E' + BD'E + ACE$

3-5 PRODUCT OF SUMS SIMPLIFICATION

- The minimized Boolean functions derived from the map in all previous examples were expressed in the sum of products form.
- With a minor modification, the product of sum form can be obtained.
- The procedure for obtaining a minimized function in product of sums follows from the basic properties of Boolean functions.
- The 1's placed in the squares of the map represent the minterms of the function.

- If we mark the empty squares by 0's and combine them into valid adjacent squares, we obtain a simplified expression of the complement of the function.
- The complement of the complement of the function (F') gives us back the function F .
- Because of the generalized DeMorgan's theorem, the function so obtained is automatically in the product of sums form.
- **Example 3-8**
- Simplify the following Boolean function in (a) sum of products and (b) product of sums.
 - $F(A, B, C, D) = \sum(0, 1, 2, 5, 8, 9, 10)$
- The 1's marked in the map of Fig 3-14 represent all the minterms of the function.

 


FIGURE 3-14

Map for Example 3-8; $F(A, B, C, D) = \Sigma (0, 1, 2, 5, 8, 9, 10) = B'D' + B'C' + A'C'D = (A' + B')(C' + D')(B' + D)$

- The squares marked with 0's represent the minterms not included in F and, therefore, denote the complement of F.
- Combining the squares with 1's gives the simplified function in sum of products:
 - (a) $F = B'D' + B'C' + A'C'D$
- If the squares marked with 0's are combined, as shown in the diagram, we obtain the simplified complemented function:
 - $F' = AB + CD + BD'$
- Applying DeMorgan's theorem (by taking the dual and complement each literal), we obtain the simplified function in product of sums:
 - $F = (A' + B')(C' + D')(B' + D)$

•The implementation of the simplified expression obtained in Example 3-8 is shown in Fig 3-15.

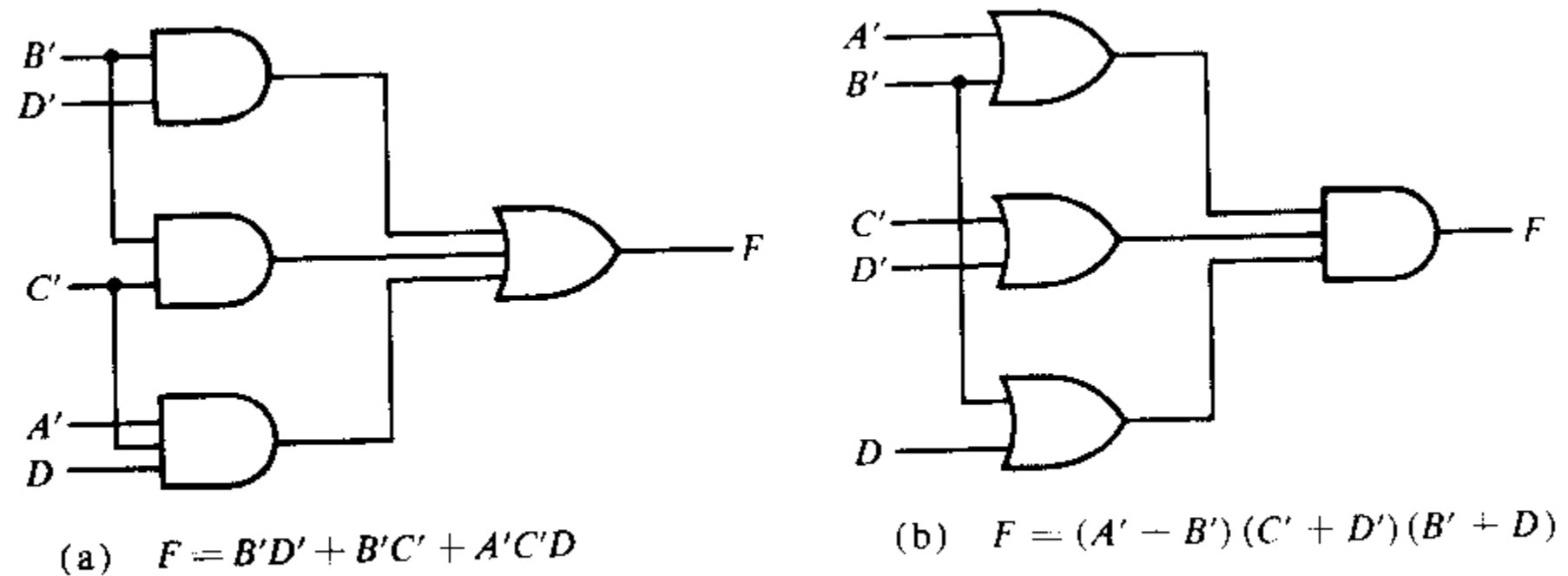


FIGURE 3-15

Gate implementation of the function of Example 3-8

- The sum of products expression is implemented in (a) with a group of AND gates, one for each AND term.
- The outputs of the AND gates are connected to the inputs of a single OR gate.
- The same function is implemented in (b) in its product of sums form with a group of OR gates, one for each OR term.
- The outputs of the OR gates are connected to the inputs of a single AND gates.
- In each case, it is assumed that the input variables are directly available in their complement, so inverters are not needed.
- The configuration pattern established in Fig 3-15 is the general form by which any Boolean function is implemented when expressed in one of the standard forms.

- AND gates are connected to a single OR gate when in sum of products.
- OR gates are connected to a single AND gate when in product of sums.
- Either configuration form two level of gates.
- Therefore, the implementation of a function in a standard form is said to be a two-level implementation.
- Example 3-8 showed the procedure for obtaining the products of sum simplification when the function is expressed in sum of minterms canonical form.
- The procedure is also valid when the function is originally expressed in product of maxterms canonical form.
- Consider, for example, the truth table that defines the function F in Table 3-2.

TABLE 3-2
Truth Table of Function F

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

- In sum of minterms, this function is expressed as
 - $F(x, y, z) = \sum(1, 3, 4, 6)$
- In product of maxterms, it is expressed as
 - $F(x, y, z) = \prod(0, 2, 5, 7)$
- The 1's in the function represent the minterms, and the 0's represent the maxterms.
- The map for this function is shown in Fig 3-16.

		yz		y	
		00	01	11	10
x	0	0	1	1	0
x	1	1	0	0	1
		z			

FIGURE 3-16

Map for the function of Table 3-2

- One can start simplifying this function by first marking the 1's for each minterm that function is a 1.
- The remaining squares are marked by 0's.
- If, however, the product of maxterms is initially given, one can start marking 0's in those squares in the function.

- The remaining squares are then marked by 1's.
- Once the 1's and 0's are marked, the function can be simplified in either one of the standard forms.
- For the sum of products, we combine the 1's to obtain
 - $F = x'z + xz'$
- For the product of sums, we combine the 0's to obtain the simplified complemented function:
 - $F' = xz + x'z'$
- Which shows that the exclusive-OR function is the complement of the equivalence function.
- Taking the complement of F' , we obtain the function in product of sums:
 - $F = (x' + z')(x + z)$



- To enter a function expressed in product of sums in the map, take the complement of the function and from it find the squares to be marked by 0's.
- For example, the function
 - $F = (A' + B' + C')(B + D)$
- can be entered in the map by first taking its complement:
 - $F' = ABC + B'D'$
- And then marking 0's in the squares representing the minterms of F' .
- The remaining squares are marked by 1's.

Exercises



- Simplify the following using a four variable map.
 - $F(w, x, y, z) = \sum(0, 1, 2, 3, 4, 5, 7, 11, 15)$
- Simplify the following Boolean expression using a four-variable map.
 - $F = w'z + xz + x'y + wx'z$
- Find the minterms of the following Boolean function
 - $F = xy + yz + xy'z$
- Simplify the following Boolean function using a five-variable map
 - $F(A, B, C, D, E) = \sum(0, 2, 3, 4, 5, 6, 7, 11, 15, 16, 18, 19, 23, 27, 31)$

  3-6 NAND AND NOR IMPLEMENTATION


- Digital circuits are more frequently constructed with NAND or NOR gates than with AND and OR gates.
- NAND and NOR gates are easier to fabricate with electronic components and are the basic gates used in all IC digital logic circuits.
- Rules and procedures have been developed for the conversion from Boolean functions given in terms of AND, OR, and NOT into equivalent NAND and NOR diagrams.
- To facilitate the conversion to NAND and NOR logic, it is convenient to define two other graphic symbols for these gates.
- Two equivalent symbols for the NAND gate are shown in Fig 3-17(a).



(a) Two graphic symbols for NAND gate.

  

(b) Two graphic symbols for NOR gate.

 


(c) Three graphic symbols for inverter.

FIGURE 3-17


Graphic symbols for NAND and NOR gates

- The AND-invert symbol has been defined previously and consists of an AND graphic symbol followed by a small circle.
- Instead, it is possible to represent a NAND gate by an OR graphic symbol preceded by small circles in all inputs.
- The invert-OR symbol for the NAND gate follows from DeMorgan's theorem and from the convention that small circles denote complementation.
- Similarly, there are two graphic symbols for the NOR gate, as shown in Fig. 3-17(b).
- The OR-invert is the conventional symbol.
- But using DeMorgan's theorem, we come up with the Invert-AND symbol.
- A one input NAND or NOR gate behaves like an inverter.


- An inverter gate can be drawn in three different ways (Fig 2-17(c)).
- The small circles in all inverter symbols can be transferred to the input terminal without changing the logic of the gate.
- NAND implementation**
- The implementation of a Boolean function with NAND gates requires that the function be simplified in the sum of products form.
- To see the relationship between the sum of products expression and its equivalent NAND implementation, consider Fig 3-18.

 

(a) AND-OR

 

(b) NAND-NAND

 

(c) NAND-NAND

FIGURE 3-18

Three ways to implement $F = AB + CD + E$

- All three diagrams are equivalent and implement the function:
 - $F = AB + CD + E$
- The function is implemented in Fig. 3-18(a) in sum of products form with AND and OR gates.
- In (b) the AND gates are replaced by NAND gates and the OR gate is replaced by a NAND gate with an invert-OR symbol.
- The single E variable E is complemented and applied to the second-level invert-OR gate.
- Two circles on the same line represent double complementation and both can be removed.
- The complement of E goes through a small circle that complements the variable again to produce the normal value of E.

- Removing the small circles in the gates of Fig. 3-18(b) produces the circuit in (a).
- Therefore, the two diagrams implement the same function and are equivalent.
- In Fig 3-18(c), the output NAND gate is redrawn with the conventional symbol.
- The one-input NAND gate complements variable E.
- It is possible to remove this inverter and apply E' directly to the input of the second-level NAND gate.
- The diagram in (c) is equivalent to the diagram in (b), which in turn is equivalent to the diagram in (a).
- The NAND implementation in Fig 3-18(c) can be verified algebraically.

- The NAND function it implements can be easily converted to a sum of products form by using DeMorgan's theorem:

- $$F = [(AB)' \cdot (CD)' \cdot E']' = AB + CD + E$$

- Hence, a Boolean function can be implemented with two-level of NAND gate, known as two-level implementation.

- The rule for obtaining the NAND logic diagram from a Boolean function is as follows:

- 1. Simplify the function and express it in sum of products.

- 2. Draw a NAND gate for each product term of the function that has at least two literals

- The inputs to each NAND gate are the literals of the term.

- This constitutes a group of first-level gates.

- 3. Draw a single NAND gate (using the AND-invert or invert-OR graphic symbol) in the second level.
 - The inputs to this NAND gate comes from the outputs of first-level gates.
- 4. A term with a single literal requires an inverter in the first level or may be complemented and applied as an input to the second-level NAND gate.
- Example 3-9**
- Implement the following function with NAND gates:
 - $F(x, y, z) = \sum(0, 6)$
- The first step is to simplify the function in sum of products form.
- This is attempted with the map shown in Fig. 3-19(a).

		yz		y	
		00	01	11	10
x	0	1	0	0	0
x	1	0	0	0	1


z

$$F = x'y'z' + xyz'$$


$$F' = x'y + xy' + z$$

 (a) Map simplification in sum of products.

- There are only two 1's in the map, and they can not be combined.
- The simplified function in sum of products for this example is
 - $F = x'y'z' + xyz'$
- The two level NAND gate implementation is shown in Fig 3-19(b).



$$(b) F = x'y'z' + xyz'$$

 

$$(c) F' = x'y + xy' + z$$


FIGURE 3-19

Implementation of the function of Example 3-9 with NAND gates


- Next we try to simplify the complement of the function in sum of products.
- This is done by combining the 0's in the map:
 - $F' = x'y + xy' + z$
- The two-level NAND gate for generating F' is shown in Fig. 3-19 (c).
- If output F is required, it is necessary to add a one-input NAND gate to invert the function.
- This gives a three-level implementation.
- The one-input NAND gate associated with the single variable z can be removed provided the input is changed to z' .

•NOR IMPLEMENTATION


- The NOR function is the dual of the NAND function.
- For this reason, all procedures and rules for NOR logic are the duals of the corresponding procedures and rules developed for NAND logic.
- The implementation of a Boolean function with NOR gates requires that the function be simplified in product of sums form
- A product of sums expression specifies a group of OR gates for the sum terms, followed by an AND gate to produce the product.
- The transformation from the OR-AND to the NOR-NOR diagram is depicted in Fig 3-20.
- It is similar to the NAND transformation discussed previously, except that now we use the product of sums expression
$$F = (A + B)(C + D)E$$

 

(a) OR-AND

 

(b) NOR-NOR

 

(c) NOR-NOR

FIGURE 3-20

Three ways to implement $F = (A + B)(C + D)E$

- The rule for obtaining the NOR logic diagram from a Boolean function can be derived from this transformation.
- It is similar to the three-step NAND rule, except that the simplified expression must be in the product of sums.
- And the terms for the first-level NOR gates are sum terms.
- A term with a single literal requires a one-input NOR or inverter gate or may be complemented and applied directly to the second-level NOR gate.
- A second way to implement a function with NOR gates would be to use the expression for the complement of the function in product of sum.
- This will give a two-level implementation for F' and a three-level implementation if the normal output F is required.

- **Example 3-10**
- Implement the function of Example 3-9 with NOR gates.
 - $F(x, y, z) = \sum(0, 6)$

		<i>yz</i>		<i>y</i>	
		00	01	11	10
<i>x</i>	0	1	0	0	0
<i>x</i>	1	0	0	0	1
		<i>z</i>			

$$F = x'y'z' + xyz'$$

$$F' = x'y + xy' + z$$

(a) Map simplification in sum of products.

- We combine the 0's in the map to obtain

- $F' = x'y + xy' + z$


- This is the complement of the function in sum of products.

- Complement F' to obtain


- $F = (x + y')(x' + y)(z')$

- As required for NOR implementation.

 - The two-level implementation with NOR gates is shown in Fig 3-12 (a).



(a) $F = (x + y')(x' + y)z'$

 

(b) $F' = (x + y + z)(x' + y' + z)$

FIGURE 3-21

Implementation with NOR gates

- A second implementation is possible from the complement of the function in product of sums.
- For this case, first combine the 1's in the map to obtain
 - $F = x'y'z' + xyz'$
- This is the simplified expression in sum of products.
- Complement this function to obtain the complement of the function in product of sums as required for NOR implementation:
 - $F' = (x + y + z)(x' + y' + z)$
- The two-level implementation for F' is shown in Fig 3-21 (b).
- If output F is desired, it can be generated with an inverter in the third level.

- Table 3-3 summarizes the procedures for NAND or NOR implementation.
- We should always remember to simplify the function in order to reduce the number of gates in the implementation.

TABLE 3-3
Rules for NAND and NOR Implementation

Case	Function to simplify	Standard form to use	How to derive	Implement with	Number of levels to F
(a)	F	Sum of products	Combine 1's in map	NAND	2
(b)	F'	Sum of products	Combine 0's in map	NAND	3
(c)	F	Product of sums	Complement F' in (b)	NOR	2
(d)	F'	Product of sums	Complement F in (a)	NOR	3

3-7 OTHER TWO-LEVEL IMPLEMENTATIONS


- **Nondegenerate Forms**

- We will consider all the possible two-level combinations of gates.
- We consider four types of gates: AND, OR, NAND and NOR.
- If we assign one type of gate for the first level and one type for the second level, we find that there are 16 possible combinations of two-level forms.
- The same type of gate can be in the first and second levels, as in NAND-NAND implementation.
- Eight of these combinations are said to be degenerate forms because they degenerate to a single operation.


- This can be seen from a circuit with AND gates in the first level and an AND gate in the second level.
- The output of the circuit is merely the AND function of all input variables.
- The other eight nondegenerate forms produce an implementation in sum of products or product of sums.
- The eight nondegenerate forms are:

• AND-OR	OR-AND
• NAND-NAND	NOR-NOR
• NOR-OR	NAND-AND
• OR-NAND	AND-NOR
- The first gate listed in each of the forms constitutes a first level in the implementation.
- The second gate listed is a single gate placed in the second level


- Note that any two forms listed in the same line are the duals of each other.
- The AND-OR and OR-AND forms and the NAND-NAND and NOR-NOR were discussed earlier.
- The remaining four forms are investigated in this section.
- AND-OR-INVERT Implementation**
- The two forms NAND-AND and AND-NOR are equivalent and can be treated together.
- Both perform the AND-OR-INVERT function, as shown in Fig. 3-23.

 

(a) AND-NOR

 

(b) AND-NOR,

 

(c) NAND-AND

FIGURE 3-23


AND-OR-INVERT circuits; $F = (AB + CD + E)'$

- The AND-NOR form resembles the AND-OR form with an inversion done by the small circle in the output of the NOR gate.
- It implements the function
 - $F = (AB + CD + E)'$
- By using the alternate graphic symbol for the NOR gate, we obtain the diagram of Fig. 3-23(b).
- Note that the single variable E is not complemented because the only change made is in the graphic symbol of the NOR gate.
- Now we move the circles from the input terminal of the second-level gate to the output terminals of the first-level gates.
- An inverter is needed for the single variable to maintain the circle.
- Alternatively, the inverter can be removed as long we complement E.


- The circuit of Fig. 3-23(c) is a NAND-AND form.
- An AND-OR implementation requires an expression in sum of products.
- The AND-OR-INVERT implementation is similar except for the inversion.
- Therefore, first the complement of the function is simplified in sum of products (by combining the 0's in the map).
- Then it will be possible to implement F' with AND-OR part of the function.
- When F' passes through the always present output inversion (the INVERT part), it will generate the output F of the function.

•OR-AND-INVERT Implementation

 
- The OR-NAND and NOR-OR forms perform the OR-AND-INVERT function. As depicted in Fig 3-24.



(a) OR-NAND

 

(b) OR-NAND

 

(c) NOR-OR

FIGURE 3-24

OR-AND-INVERT circuits; $F = [(A + B)(C + D)E]'$

- The OR-NAND form resembles the OR-AND form, except for the inversion done by the circle in the NAND gate.
- It implements the function:
 - $F = [(A + B)(C + D)E]'$
- By using the alternate graphic symbol for the NAND gate, we obtain the diagram of Fig 3-24(b).
- The circuit in (c) is obtained by moving the small circles from the inputs of the second-level gate to the outputs of the first level gates.
- The circuit of Fig. 3-24(c) is a NOR-OR form.
- The OR-AND-INVERT implementation requires an expression in product of sums.

- If the complement of the function is simplified in product of sums, we can implement F' with the OR-AND part of the function.
- When F' passes through the INVERT part, we obtain the complement F' , or F , in the output.
- **Tabular Summary and Example**
- Table 3-4 summarizes the procedures for implementing a Boolean function in any one of the four two-level forms.
- Because of the INVERT part in each case, it is convenient to use the simplification of F' (the complement) of the function.
- When F' is implemented in one of these forms, we obtain the complement of the function in the AND-OR or OR-AND form
- The four two level forms invert this function, giving an output that is the complement of F' (F).


TABLE 3-4
Implementation with Other Two-Level Forms

Equivalent nondegenerate form		Implements the function	Simplify F' in	To get an output of
(a)	(b)*			
AND-NOR	NAND-AND	AND-OR-INVERT	Sum of products by combining 0's in the map	F
OR-NAND	NOR-OR	OR-AND-INVERT	Product of sums by combining 1's in the map and then complementing	F

*Form (b) requires a one-input NAND or NOR (inverter) gate for a single literal term.

 Example 3-11


- Implement the function $F = x'y'z' + xyz'$ in the four two-level forms.
- The karnaugh map for the function is shown.



 
(a) Map simplification in sum of products.

- The complement of the function is simplified in sum of products by combining the 0's in the map.
- $F' = x'y + xy' + z$

- The normal output for this function can be expressed as
 - $F = (x'y + xy' + z)'$
- Which is in the AND-OR-INVERT form.
- The AND-NOR and NAND-AND implementations are shown in Fig. 3-25(a).




AND-NOR

 


NAND-AND

 (a) $F = (x'y + xy' + z)'$

- Note that a one-input NAND or inverter gate is needed in the NAND-AND implementation, but not in the AND-NOR case.
- The OR-AND-INVERT forms require a simplified expression of the complement of the function in product of sums.
- To obtain this expression, we must first combine the 1's in the map
 - $F = x'y'z' + xyz'$
- Then we take the complement of the function
 - $F' = (x + y + z)(x' + y' + z)$
- The normal output F can now be expressed in the form
 - $F = [(x + y + z)(x' + y' + z)]'$
- Which is in the OR AND-INVERT form. From this expression we can implement the function in OR-NAND and NOR-OR forms as shown in Fig 3-25(b).



OR-NAND

 

NOR-OR

$$(b) F = [(x + y + z)(x' + y' + z)]'$$

FIGURE 3-25

Other two-level implementations

•Exercises

•1-Simplify the following expressions and implement it with two-level NAND gate circuits:

• $F = BD + BCD' + AB'C'D$

•2-Simplify the following function and implement it with three-level NOR gate circuit:

$F = wx' + y'z' + w'yz'$

•3. Simplify and implement Problem no.2 with two level NOR gate circuit.

•3. Implement the function F with the following two-level forms: NAND-AND, AND-NOR, OR-NAND and NOR-OR.

• $F(A, B, C, D) = \sum(0, 1, 2, 3, 4, 8, 9, 12)$

3-8 DON'T-CARE CONDITIONS

- The logical sum of the minterms associated with a Boolean function specifies the condition under which the function is equal to 1.
- The function is equal to 0 for the rest of the minterms.
- This assumes that all the combinations of the values for the variables of the function are valid.
- In practice, there are some applications where the function is not specified for certain combinations of the variables.
- As an example, the four-bit binary code for the decimal digits has six combinations that are not used and consequently are considered unspecified.
- Functions that have unspecified outputs for some input combinations are called incompletely specified functions.


- In most applications, we simply don't care what value is assumed by the function for the unspecified minterms.
- For this reason, it is customary to call the unspecified minterms of a function don't care conditions.
- These don't-care conditions can be used on the map to provide further simplification of the Boolean expression.
- It should be noted that don't-care minterm is a combination of variables whose logical value is not specified.
- It cannot be marked with a 1 in the map because it would require that the function be 1 for such combination.
- Similarly, putting a 0 on the square requires the function be 0.

- To distinguish the don't-care condition from 1's and 0's, an X is used.
- Thus, an X inside a square in the map indicates that we don't care whether the value of 0 or 1 is assigned to F for the particular minterm.
- When choosing adjacent squares to simplify the function in the map, the don't care minterms may be assumed to be either 0 or 1.
- When simplifying the function, we can choose to include each don't care minterm with either the 1's or the 0's, depending on which combination gives the simplest expression.

 
• **Example 3-12**

- Simplify the Boolean function
 - $F(w, x, y, z) = \sum(1, 3, 7, 11, 15)$
- That has the don't-care conditions
 - $d(w, x, y, z) = \sum(0, 2, 5)$

- The minterms of F are the variable combinations that make the function equal to 1.
- The minterms of d are the don't-care minterms that may be assigned either 0 or 1.
- The map simplification is shown in Fig. 3-26.



(a) $F = yz + w'x'$

 

(b) $F = yz + w'z$

FIGURE 3-26

Example with don't-care conditions

- The minterms of F are marked by 1's, those of d are marked by X's, and the remaining squares are filled with 0's.
- To get the simplified expression in sum of products, we must include all the five 1's in the map.
- But we may or may not include any of the X's, depending on the way the function is simplified.
- The term yz covers the four minterms in the third column.
- The remaining minterm m_1 can be combined with minterm m_3 to give the three-literal term $w'x'z$.
- However, by including one or two adjacent X's we can combine four adjacent squares to give a two-literal form.

- In part (a) of the diagram, don't-care minterms 0 and 2 are included with 1's, which results in the simplified function

- $F = yz + w'x'$

- In part (b), don't-care minterm 5 is included with the 1's and the simplified function now is

- $F = yz + w'z$

- Either one of the above expressions satisfies the conditions states for this example.

- The above example has shown that the don't-care minterms in the map are initially marked with X's and are considered as being either 0 or 1.

- The choice between 0 and 1 is made depending on the way the incompletely specified function is simplified.

- Once the choice is made, the simplified function so obtained will consist of a sum of minterms that includes those minterms that were initially unspecified and have been chosen to be included with the 1's.
- Consider the two simplified expressions obtained in Example 3-12:
 - $F(w, x, y, z) = yz + w'x' = \sum(0, 1, 2, 3, 7, 11, 15)$
 - $F(w, x, y, z) = yz + w'z = \sum(1, 3, 5, 7, 11, 15)$
- Both expressions include minterms 1, 3, 7, 11 and 15 that make the function equal to 1.
- The don't-care minterms 0, 3, and 5 are treated differently in each expression.
- The first expression includes minterms 0 and 2 with the 1's and leaves minterm 5 with the 0's.

- The second expression includes minterm 5 with 1's and leaves minterms 0 and 2 with the 0's.
- The two expressions represent two functions that are algebraically unequal.
- Both cover the specified minterms of the function, but each covers different don't-care minterms.
- As far as the incompletely specified function is concerned, either expression is acceptable since the only difference is in the value of F for the don't-care minterms.
- It is also possible to obtain a simplified product of sums expression for the function of Fig. 3-26.
- In this case , the only way to combine the 0's is to include don't-care minterms 0 and 2 with the 0's to give a simplified complemented function:
 - $F' = z' + wy'$

- Taking the complement of F' gives the simplified expression in product of sums:

- $F(w, x, y, z) = z'(w + y') = \sum(1, 3, 5, 7, 11, 15)$

- For this case, we include minterms 0 and 2 with the 0's and minterm 5 with 1's.

• 3-9 THE TABULATION METHOD

- The map method of simplification is convenient as long as the number of variables does not exceed five or six.

- As the number of variables increases, the excessive number of squares prevents a reasonable selection of adjacent squares.

- The obvious disadvantage of the map is that it is essentially trial-and-error procedure that relies on the ability of the human to recognize certain patterns.

- For functions of six or more variables, it is difficult to be sure that the best selection has been made.

- The tabulation method overcomes this difficulty.
- It is a specific step-by-step procedure that is guaranteed to produce a simplified standard-form expression for a function.
- It can be applied to problems with many variables and has the advantage of being suitable for machine computation.
- However, it is quite tedious for human use and is prone to mistakes because of its routine process.
- The tabulation method was first formulated by Quine and later improved by McCluskey.
- It is also known as the Quine-McCluskey method.

3-10 DETERMINATION OF PRIME IMPLICANTS

- The starting point of the tabulation method is the list of minterms that specify the function.
- The first tabular operation is to find the prime implicants by using a matching process.
- This process compares each minterm with every other minterm.
- If two minterms differ in only one variable, that variable is removed and a term with one less literal is found.
- This process is repeated for every minterm until the exhaustive search is completed.
- The matching-process cycle is repeated for those new terms just found.

- Third and further cycles are continued until a single pass through a cycle yields no further elimination of literals.
- The remaining terms and all the terms that did not match during the process comprise the prime implicants.

Example 3—13

Simplify the following Boolean function by using the tabulation method.

$$F(w, x, y, z) = \sum(0, 1, 2, 8, 10, 11, 14, 15)$$

Step1: Group binary representation of the minterms according to the number of 1's contained, as shown in Table 3-5, column (a).

TABLE 3-5
Determination of Prime Implicants for Example 3-13

(a)	(b)	(c)
$w x y z$	$w x y z$	$w x y z$
0 0 0 0 0 ✓	0, 1 0 0 0 –	0, 2, 8, 10 – 0 – 0
	0, 2 0 0 – 0 ✓	0, 8, 2, 10 – 0 – 0
1 0 0 0 1 ✓	0, 8 – 0 0 0 ✓	10, 11, 14, 15 1 – 1 –
2 0 0 1 0 ✓		10, 14, 11, 15 1 – 1 –
8 1 0 0 0 ✓	2, 10 – 0 1 0 ✓	
	8, 10 1 0 – 0 ✓	
10 1 0 1 0 ✓	10, 11 1 0 1 – ✓	
11 1 0 1 1 ✓	10, 14 1 – 1 0 ✓	
14 1 1 1 0 ✓	11, 15 1 – 1 1 ✓	
15 1 1 1 1 ✓	14, 15 1 1 1 – ✓	

This is done by grouping the minterms into five sections separated by horizontal lines.

- The first section contains the number with no 1's in it.'
- The second section contains those numbers that have only one 1.
- The third, fourth, and fifth sections contain those binary numbers with two, three, and four 1's, respectively.
- The decimal equivalents of the minterms are also carried along for identification.
- Step 2: Any two minterms that differ from each other by only one variable can be combined, and the unmatched variable removed.
- Two minterm numbers fit into this category if they both have the same bit value in all positions except one.

- The minterms in one section are compared with those of the next section down only, because two terms differing by more than one bit cannot match.
- The minterm in the first section is compared with each of the three minterms in the second section.
- If any two numbers are the same in every position but one, a check is placed to the right of both minterms to show that they have been used.
- The resulting term, together with the decimal equivalent of the selected minterms, is listed in column (b) of the table.
- The variable eliminated during the matching is denoted by a dash in its position.
- In this case, $m_0(0000)$ combines with $m_1(0001)$ to form $(000-)$.

- This combination is equivalent to the algebraic operation
 - $m_0 + m_1 = w'x'y'z' + w'x'y'z = w'x'y'$
- Minterm m_0 also combines with m_2 to form (00 -0) and with m_8 to form (-000).
- The result of this comparison is entered into the first section of column (b).
- The minterms of sections two and three of column (a) are next compared to produce the terms listed in the second section of column (b).
- All other section of (a) are similarly compared and subsequent sections formed in (b).
- This exhaustive comparing process results in the four sections of (b).
- Step 3:
- The terms of column (b) have only three variables.

- A 1 under the variable means it is unprimed, a 0 means it is primed, and a dash means the variable is not included in the term.
- The searching and comparing process is repeated for the terms in column (b) to form the two-variable terms of column (c).
- Again, terms in each section need to be compared only if they have dashes in the same position.
- Note that the term (000-) does not match with any other term.
- Therefore, it has no check mark at its right.
- The decimal equivalents are written on the left-hand side of each entry for identification purposes.
- The comparing process should be carried again in column (c) and in subsequent columns as long as proper matching is encountered.

- In the present example, the operation stops at the third column.
- Step 4:
- The unchecked terms in the table form the prime implicants.
- In this example, we have the term $w'x'y'$ (000_) in column (b), and the terms $x'z'$ (-0-0) and wy (1-1-) in column (c).
- Note that each term in column (c) appears twice in the table, and as long as the term forms a prime implicant, it is unnecessary to use the same term twice.
- The sum of the prime implicants gives a simplified expression for the function.
- This is because each checked term in the table has been taken into account by an entry of a simpler term in subsequent column.
- Therefore, the unchecked entries (prime implicants) are the terms left to formulate the function.

- For the present example, the sum of prime implicants gives the minimized function in sum of products:

- $$F = w'x'y' + x'z' + wy$$

- It is worth comparing this answer with that obtained by the map method.

- Figure 3-27 shows the map simplification of this function.

 


FIGURE 3-27

Map for the function of Example 3-13;

$$F = w'x'y' + x'z' + wy$$

- The combinations of adjacent squares give the three prime implicants of the function.
- The sum of these three terms is the simplified expression in sum of products.
- The work when using the tabulation method is reduced if the comparing is done with decimal numbers instead of binary.
- A method will be used that uses subtraction of decimal numbers instead of the comparing and matching of binary numbers.
- We note that each 1 in a binary number represents the coefficient multiplied by a power of 2.
- When two minterms are the same in every position except one, the minterm with the extra 1 must be larger than the number of the other minterm by a power of 2.

- Therefore, two minterms can be combined if the number of the first minterm differs by a power of 2 from a second larger number in the next section down the table.
- We shall illustrate this procedure by repeating Example 3-13.
- As shown in Table 3-6, column (a), the minterms are arranged in sections as before except that now only the decimal equivalents of the minterms are listed.
- The process of comparing minterms is as follows: Inspect every two decimal numbers in adjacent sections of the table.
- If the number in the section below is greater than the number in the section above by a power of 2 (i.e., 1, 2, 4, 8, 16, etc), check both numbers to show that they have been used, and write them down in column (b).

- The pair of numbers transferred to column (b) includes a third number in parentheses that designates the power of 2 by which the numbers differ.
- The number in parenthesis also tells us the position of the dash in the binary notation.
- The results of all comparisons of column (a) are shown in column (b).
- The comparison between adjacent sections in column (b) is carried out in a similar fashion, except that only those terms with the same number in parenthesis are compared.
- The pair of numbers in section must differ by a power of 2 from the pair of numbers in the next section.
- And the numbers in the next section below must be greater for the combination to take place.

- In column (c), write all four decimal numbers with the two numbers in parentheses designating the positions of the dashes.

TABLE 3-6**Determination of Prime Implicants of Example 3-13 with Decimal Notation**

(a)	(b)	(c)
<u>0</u> ✓	0, 1 (1)	0, 2, 8, 10 (2, 8)
	0, 2 (2) ✓	<u>0, 2, 8, 10 (2, 8)</u>
1 ✓	<u>0, 8 (8) ✓</u>	
2 ✓		10, 11, 14, 15 (1, 4)
<u>8</u> ✓	2, 10 (8) ✓	<u>10, 11, 14, 15 (1, 4)</u>
	<u>8, 10 (2) ✓</u>	
<u>10</u> ✓		
	10, 11 (1) ✓	
11 ✓	<u>10, 14 (4) ✓</u>	
<u>14</u> ✓		
	11, 15 (4) ✓	
15 ✓	14, 15 (1) ✓	

- The prime implicants are those terms not checked in the table.
- These are the same as before, except that they are given decimal notation.
- To convert from decimal notation to binary , convert all decimal numbers in the term to binary and then insert a dash in those positions designated by the numbers in parentheses.
- Thus 0, 1 (1) is converted to binary as 0000, 0001; a dash in the first position of either number results in (000--).
- Similarly, 0, 2, 8, 10 (2, 8) is converted to the binary notation from 0000, 0010, 1000, and 1010, and a dash inserted in positions 2 and 8, to result in (-- 0 --0).

•Example 3-14

•Determine the prime implicants of the function.

$$•F(w, x, y, z) = \sum(1, 4, 6, 7, 8, 9, 10, 11, 15)$$

- The minterms are grouped in sections, as shown in Table 3-7, column (a).
- The binary equivalent of the minterm is included for the purpose of counting the number of 1's.
- The binary numbers in the first section have only one 1, in the second section, two 1's, etc.

TABLE 3-7
Determination of Prime Implicants for Example 3-14

(a)			(b)			(c)
0001	1	✓	1, 9	(8)		8, 9, 10, 11 (1, 2)
0100	4	✓	4, 6	(2)		8, 9, 10, 11 (1, 2)
1000	8	✓	8, 9	(1)	✓	
			8, 10	(2)	✓	
0110	6	✓				
1001	9	✓	6, 7	(1)		
1010	10	✓	9, 11	(2)	✓	
			10, 11	(1)	✓	
0111	7	✓				
1011	11	✓	7, 15	(8)		
			11, 15	(4)		
1111	15	✓				

Prime implicants

Decimal	Binary				Term
	w	x	y	z	
1, 9 (8)	—	0	0	1	$x'y'z$
4, 6 (2)	0	1	—	0	$w'xz'$
6, 7 (1)	0	1	1	—	$w'xy$
7, 15 (8)	—	1	1	1	xyz
11, 15 (4)	1	—	1	1	wyz
8, 9, 10, 11 (1, 2)	1	0	—	—	wx'

- The minterm numbers are compared by the decimal method and a match is found if the number in the section below is greater than that in the section above.
- If the number in the section below is smaller than the one above, a match is not recorded even if the two numbers differ by a power of 2.
- The exhaustive search in column (a) results in the terms of column (b), with all minterms in column (a) being checked.
- There are only two matches of terms in column (b).
- Each gives the same two literal term recorded in column (c).
- The prime implicants consists of all the unchecked terms in the table.
- The conversion from the decimal to the binary notation is shown at the bottom of the table.

- The prime implicants are found to be $x'y'z$, $w'xz'$, $w'xy$, xyz , wyz , and wx' .
- The sum of the prime implicants gives a valid algebraic expression for the function.
- However, this expression is not necessarily the one with the minimum number of terms.
- This can be demonstrated from inspection of the map for the function of Example 3-14.
- As shown in Fig 3-28, the minimized function is recognized to be
 - $F = x'y'z + w'xz' + xyz + wx'$
- Which consists of the sum of four of the six prime implicants derived in Example 3-14.

- The tabular procedure for selecting the prime implicants that give the minimized function is the subject of the next section.

 


FIGURE 3-28
 Map for the function of Example 3-14;
 $F = x'y'z' + w'xz' + xyz + wx'$

3-11 SELECTION OF PRIME IMPLICANTS

- The selection of prime implicants that form the minimized function is made from a prime implicant table.
- In this table, each prime implicant is represented in a row and each minterm in a column.
- X's are placed in each row to show the composition of minterms that make the prime implicants.
- A minimum set of prime implicants is then chosen that covers all the minterms in the function.
- This procedure is illustrated in Example 3-15.

Example 3-15

- Minimize the function in Example 3-14.
- The prime-implicant table for this example is shown in Table 3-8.

TABLE 3-8
Prime Implicant Table for Example 3-15

		1	4	6	7	8	9	10	11	15
$\sqrt{x'y'z}$	1, 9	X					X			
$\sqrt{w'xz'}$	4, 6		X	X						
$w'xy$	6, 7			X	X					
xyz	7, 15				X					X
wyz	11, 15								X	X
$\sqrt{wx'}$	8, 9, 10, 11					X	X	X	X	
		\checkmark	\checkmark	\checkmark		\checkmark	\checkmark	\checkmark	\checkmark	

- There are six rows, one for each prime implicant (derived in Example 3-14).
- There are nine columns, each representing one minterm of the function.
- X's are placed in each row to indicate the minterms contained in the prime implicant of that row.
- For example, the two X's in the first row indicate that minterms 1 and 9 are contained in the prime implicant $x'y'z$.
- It is advisable to include the decimal equivalent of the prime implicants in each row, as it gives the minterms contained in it.
- After all the X's have been marked, we proceed to select a minimum number of prime implicants.

- The completed prime-implicant table is inspected for columns containing only a single X.
- In this example, there are four minterms whose columns have a single X: 1, 4, 8, and 10.
- Minterm 1 is covered by prime implicant $x'y'z$.
- Therefore, the selection of the prime implicant $x'y'z$ guarantees that minterm 1 is included in the function.
- Similarly, minterm 4 is covered by prime implicant $w'xz'$, and minterms 9 and 10, by wx' .
- Prime implicants that cover minterms with a single X in their column are called **essential prime implicants**.

- To make the final simplified version contain all the minterms, we have to include essential prime implicants.
- A check mark is placed in the table next to the essential prime implicants to indicate that they have been selected.
- Next we check each column whose minterm is covered by the selected essential prime implicants.
- For example, the selected prime implicant $x'y'z$ covers minterms 1 and 9.
- A check is inserted in the bottom of the columns.
- Similarly, prime implicant $w'xz'$ covers minterms 4 and 6, and wx' covers minterms 8, 9, 10, and 11.
- Inspection of the prime-implicant table shown that the selection of the essential prime implicants covers all the minterms of the function except 7 and 15.

- These two minterms must be included by the selection of one or more prime implicants.
- In this example, it is clear that prime implicant xyz covers both minterms and is therefore the one to be selected.
- We have thus found the minimum set of prime implicants whose sum gives the required minimized function:
 - $F = x'y'z + w'xz' + wx' + xyz$
- The simplified expression derived in the preceding example were all the sum of products form.
- The tabulation method can be adapted to give a simplified expression in product of sums.

- As in the map method, we have to start with the complement of the function by taking the 0's as the initial list of minterms.
- This list contains those minterms not included in the original function that are numerically equal to the maxterms of the function.
- The tabulation process is carried out with the 0's of the function and terminates with a simplified expression in sum of products of the complement of the function.
- By taking the complement again, we obtain the simplified product of sum expression.
- A function with don't-care conditions can be simplified by the tabulation method after a slight modification.
- The don't-care terms are included in the list of minterms, when the prime implicants are determined.

- This allows the derivation of prime implicants with the least number of literals.
- The don't-care terms are not included in the list of minterms when the prime implicant table is set up.
- The reason is that don't-care terms do not have to be covered by the selected prime implicants.

• REVIEW EXERCISES

1. Simplify the Boolean function F together with the don't care conditions d in (i) sum of products and (ii) products of sums

$$\bullet F(w, x, y, z) = \sum(0, 1, 2, 3, 7, 8, 10)$$

$$\bullet d(w, x, y, z) = \sum(5, 6, 11, 15)$$

2. Simplify the following Boolean functions by means of the tabulation method:

$$(a) P(A, B, C, D, E, F, G) = \sum(20, 28, 52, 60)$$

$$(b) P(A, B, C, D, E, F, G) = \sum(20, 28, 38, 39, 52, 60, 102, 103, 127)$$

3. Simplify the following Boolean function and draw the logic diagram of the simplified version.

$$F = xy'z + x'y'z + w'xy + wx'y + wxy$$

4. Represent the following decimal number 8620 in (a) BCD, (b) excess-3 code, (c) 2421 code

5. The binary number listed have a sign in the leftmost position and if negative, are in 2's complement form. Perform the arithmetic operations indicated and verify the answers.

a) $111001 + 001010$

b) $101011 - 100110$

6. Convert the following expression in to sum of products and product of sums
 $x' + x(x + y')(y + z')$

7. Express the following function in sum of minterms or product of maxterms
 $F(x, y, z) = (xy + z)(xz + y)$

8. Convert the following to the other canonical form
 $F(x, y, z) = \sum(1, 3, 7)$
 $F(A, B, C, D) = \prod(0, 1, 2, 3, 4, 6, 12)$