 


A high-contrast, black and white photograph of a microchip, showing a grid of circuitry and various components. The image is slightly blurred, giving it a technical and futuristic feel.


LOGIC DESIGN

Chapter 5 Synchronous
Sequential Logic


OUTLINE OF CHAPTER 5




Sequential
Circuits

 


Latches

 






Flip-flop

 

Analysis of
Clocked
Sequential Circuits

 

Design Proce-
dure

     




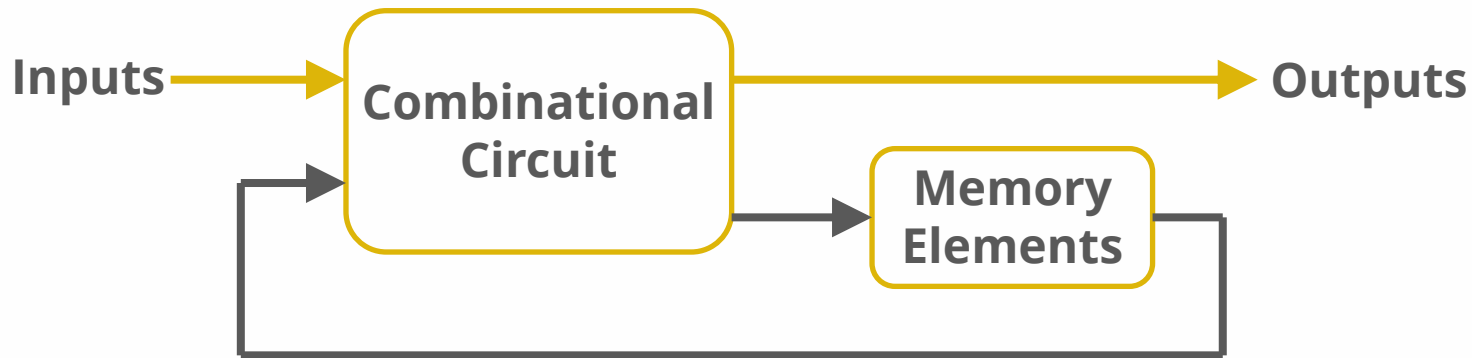5.1 SEQUENTIAL CIRCUITS

SEQUENTIAL CIRCUITS

- Every digital system is likely to have combinational circuits.
- Most systems encountered in practice also include **storage elements**, which require that the system be described in terms of **sequential logic**.



SEQUENTIAL CIRCUITS

- The storage elements are devices capable of storing binary information.
- The binary information stored in these elements at any given time defines the **state** of the sequential circuit at that time.
- The sequential circuit receives binary information from external inputs.
- These inputs, together with the present state of the storage elements, determine the binary value of the outputs.

SEQUENTIAL CIRCUITS

- They also determine the condition for changing the state in the storage elements.
- A sequential circuit is specified by a time sequence of inputs, output, and internal states.




5.2 LATCHES

LATCHES

- **Latches** are the basic circuits from which all flip – flops are constructed.
 - latches are useful for storing binary information
-

LATCHES



- SR Latch

 

S	R	Q	Q'	
1	0	1	0	Set State
0	0	1	0	Hold State
0	1	0	1	Reset State
0	0	0	1	Hold State
1	1	0	0	Invalid State

LATCHES

- SR Latch

 
 


S	R	Q	
0	0	Q_0	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q=Q'=0$	Invalid

S	R	Q	
0	0	$Q=Q'=1$	Invalid
0	1	1	Set
1	0	0	Reset
1	1	Q_0	No change

LATCHES

- SR Latch with Control Input**

  

C	S	R	Q	
0	X	X	HOLD	No change
1	0	0	HOLD	No change
1	0	1	Q = 0	Reset
1	1	0	Q = 1	Set
1	1	1	Q = Q'	Invalid


LATCHES

- **D Latch (D = Data)**

- One way to eliminate the undesirable condition of the indeterminate state in the SR latch is to ensure that inputs S and R are never equal to 1 at the same time.
- D latch has two inputs
 - D (data) - directly goes to the S input and its complement is applied to the R input.
 - C (control)


LATCHES

- D Latch (D = Data)**

 


C	D	Q	
0	X	HOLD	No change
1	0	Q = 0	Reset
1	1	Q = 1	Set

Timing Diagram

 


LATCHES

- D Latch (D = Data)**

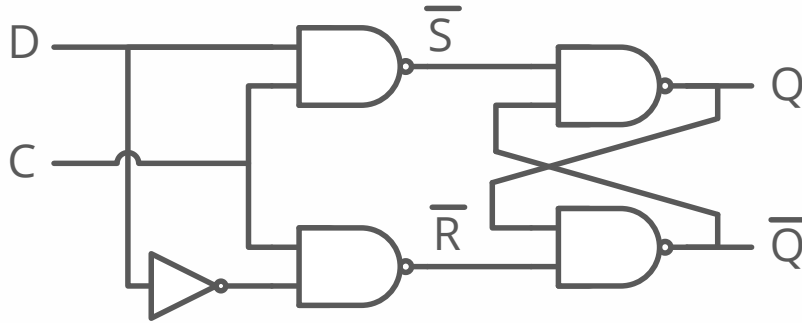

C	D	Q	
0	X	HOLD	No change
1	0	Q = 0	Reset
1	1	Q = 1	Set


Timing Diagram

 

LATCHES

- **D Latch (D = Data)**

- The D latch has an ability to hold data in its internal storage.
- It is suited for use as a temporary storage for binary information.
- This circuit is often called **transparent** latch.
 - The output follow changes in the data input as long as the control input is **enabled**.



5.3 FLIP – FLOPS

FLIP – FLOPS


- The most economical and efficient flip – flop constructed is the edge – triggered D flip – flop.
 - It requires smallest number of gates.
- Other types of flip – flops can be constructed by using the D flip – flop and external logic.
 - JK flip – flops
 - T flip - flops

FLIP – FLOPS

- There are three operations that can be performed with a flip – flop:
 - Set it to 1
 - Reset it to 0
 - Complement its output

FLIP – FLOPS

 - JK Flip – Flop
 - Performs all three operations.




$$D = JQ' + K'Q$$

- When $J = 1$, sets the flip – flop to 1.
- When $K = 1$, resets the flip – flop to 0.

FLIP – FLOPS

- JK Flip – Flop

 


$$D = JQ' + K'Q$$

Operation 1

- When $J = 1$ and $K = 0$,
 - $D = 1.Q' + 1.Q$ (Post2b)
 - $D = Q' + Q$ (Post5a)
 - $D = 1$
 - Next clock edge sets the output to 1.

FLIP – FLOPS

- JK Flip – Flop

 


$$D = JQ' + K'Q$$

Operation 2

- When $J = 0$ and $K = 1$,
 - $D = 0.Q' + 0.Q$ (Theo2b)
 - $D = 0 + 0$
 - $D = 0$
 - Next clock edge sets the output to 0.

FLIP – FLOPS

- JK Flip – Flop

 


$$D = JQ' + K'Q$$

Operation 3

- When $J = 1$ and $K = 1$,
 - $D = 1.Q' + 0.Q$ (Post2b)
 - $D = Q' + 0.Q$ (Theo2b)
 - $D = Q' + 0$ (Post2a)
 - $D = Q'$
 - Next clock edge complements the output.

FLIP – FLOPS

- JK Flip – Flop

 


$$D = JQ' + K'Q$$


- When $J = 0$ and $K = 0$,
 - $D = 0.Q' + 1.Q$ (Theo2b)
 - $D = 0 + 1.Q$ (Post2b)
 - $D = 0 + Q$ (Post2a)
 - $D = Q$
 - Next clock edge the output is unchanged.

FLIP – FLOPS

- JK Flip – Flop

 


$$D = JQ' + K'Q$$

 

FLIP – FLOPS

 - T (toggle) Flip – Flop
 - Complementing flip – flop.
 - Can be obtained from a JK flip – flop.
 - When inputs J and K are tied together.
 - Useful for designing binary counters.




$$D = JQ' + K'Q$$

$$D = TQ' + T'Q = T \oplus Q$$

FLIP – FLOPS

 - T (toggle) Flip – Flop
 - When $T = 0$ ($J = K = 0$)
 - A clock edge does not change the output.
 - When $T = 1$ ($J = K = 1$)
 - A clock edge complements the output.




$$D = JQ' + K'Q$$

$$D = TQ' + T'Q = T \oplus Q$$

FLIP – FLOPS

 
- T (toggle) Flip – Flop
 - Can be constructed with a D flip – flop and an XOR gate.
 - When $T = 0$ then $D = Q$
 - No change in the output.
 - When $T = 1$ then $D = Q'$
 - Output complements




$$D = TQ' + T'Q = T \oplus Q$$

FLIP – FLOPS


- T (toggle) Flip – Flop

 

(a) From JK Flip – Flop

 


(b) From D Flip – Flop

 

(c) Graphic Symbol

FLIP – FLOPS

- Flip – Flop Characteristics Table

 


D	Q (t+1)	
0	0	Reset
1	1	Set

$$Q(t+1) = D$$

FLIP – FLOPS

- Flip – Flop Characteristics Table

 


J	K	Q (t+1)	
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Toggle

$$Q(t+1) = JQ' + K'Q$$

FLIP – FLOPS

- Flip – Flop Characteristics Table

 

T	Q (t+1)	
0	Q(t)	No change
1	Q'(t)	Toggle

$$Q(t+1) = T \oplus Q$$



5.4 ANALYSIS OF CLOCKED SEQUENTIAL CIRCUITS

ANALYSIS OF CLOCKED SEQUENTIAL CIRCUITS

- The behaviour of a clocked sequential circuit is determined from:
 - The inputs
 - The outputs
 - The state of its flip – flops
- The outputs and the next state are both a function of
 - The inputs
 - The present state

ANALYSIS OF CLOCKED SEQUENTIAL CIRCUITS

- The analysis of sequential circuit consists of:
 - Obtaining a table or a diagram for the time sequence of
 - Inputs
 - Outputs
 - Internal states
 - It is also possible to write Boolean expression that describe the behaviour of the sequential circuit.


ANALYSIS OF CLOCKED SEQUENTIAL CIRCUITS

State Equations

- The behaviour of a clocked sequential circuit can be described algebraically by means of **state equations** (**transition equations**).
- A state equation specifies the next state as a function of
 - The present state
 - Inputs

ANALYSIS OF CLOCKED SEQUENTIAL CIRCUITS


Consider:

 

- Circuit consists of:
 - Two D flip – flops **A** and **B**.
 - An input **x**.
 - An output **y**.
 - It is possible to write a set of equations for the circuit.

ANALYSIS OF CLOCKED SEQUENTIAL CIRCUITS


Consider:

 

- $A(t+1) = A(t) \cdot x(t) + B(t) \cdot x(t)$
- $B(t+1) = A'(t) \cdot x(t)$
 - $(t+1) \rightarrow$ next state of the flip flop
 - Right side of the equation is a Boolean expression
 - Specifies the present state
 - Input conditions that make the next state = 1.

ANALYSIS OF CLOCKED SEQUENTIAL CIRCUITS


Consider:

 

- $A(t+1) = A(t) \cdot x(t) + B(t) \cdot x(t)$
- $B(t+1) = A'(t) \cdot x(t)$
 - Since all the variables in the Boolean expression are a function of the present state
 - We can omit the designation (t)
- **$A(t+1) = A \cdot x + B \cdot x$**
- **$B(t+1) = A' \cdot x$**

ANALYSIS OF CLOCKED SEQUENTIAL CIRCUITS


Consider:

 

- Similarly,
- $y(t) = [A(t) + B(t)] x'(t)$
- $y = (A + B) x'$

ANALYSIS OF CLOCKED SEQUENTIAL CIRCUITS

Consider:

 

- $A(t+1) = A \cdot x + B \cdot x$
- $B(t+1) = A' \cdot x$
- $y = (A + B) x'$

ANALYSIS OF CLOCKED SEQUENTIAL CIRCUITS

State Table


- The time sequence of inputs, outputs and flip – flop can be enumerated in **state table** (**transition table**).
- In general, a sequential circuit with m flip – flops and n inputs needs 2^{m+n} rows in the state table.

ANALYSIS OF CLOCKED SEQUENTIAL CIRCUITS

State Table

Present State (t)		Input (t)	Next State (t+1)		Output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	0	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

 - $A(t+1) = A \cdot x + B \cdot x$
- $B(t+1) = A' \cdot x$
- $y = (A + B) x'$




ANALYSIS OF CLOCKED SEQUENTIAL CIRCUITS

State Table 2

Present State (t)	Next State (t+1)		Output	
	x=0	x=1	x=0	x=1
AB	AB	AB	y	y
00	00	01	0	0
01	00	11	1	0
10	00	10	1	0
11	00	10	1	0

 - $A(t+1) = A \cdot x + B \cdot x$
- $B(t+1) = A' \cdot x$
- $y = (A + B) x'$



ANALYSIS OF CLOCKED SEQUENTIAL CIRCUITS


State Diagram

- The information available in a state table can be represented graphically in the form of a state diagram.
- State is represented by a circle
- Transition between states are indicated by directed lines connecting the circles.

ANALYSIS OF CLOCKED SEQUENTIAL CIRCUITS


State Diagram

Present State (t)	Next State (t+1)		Output	
	x=0	x=1	x=0	x=1
AB	AB	AB	y	y
00	00	01	0	0
01	00	11	1	0
10	00	10	1	0
11	00	10	1	0

 


ANALYSIS OF CLOCKED SEQUENTIAL CIRCUITS

Analysis with D Flip - Flops

 


- $A(t+1) = D_A = A \oplus x \oplus y$

 

Present state	Inputs		Next state
A	x	y	A
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

ANALYSIS OF CLOCKED SEQUENTIAL CIRCUITS

Analysis with JK Flip – Flops

 

- $J_A = B$ $K_A = B \cdot x'$
- $J_B = x'$ $K_B = A \oplus x$
- $A(t+1) = J_A Q'_A + K'_A Q_A$
 $= A'B + AB' + Ax$
- $B(t+1) = J_B Q'_B + K'_B Q_B$
 $= B'x' + ABx + A'Bx'$

ANALYSIS OF CLOCKED SEQUENTIAL CIRCUITS


Analysis with JK Flip – Flops

- $J_A = B$ $K_A = B x'$
- $J_B = x' K_B = A \oplus x$
- $A(t+1) = J_A Q'_A + K'_A Q_A$
 $= A'B + AB' + Ax$
- $B(t+1) = J_B Q'_B + K'_B Q_B$
 $= B'x' + ABx + A'Bx'$

Present State		I/P	Next State		Flip – Flop Inputs			
A	B	x	A	B	J_A	K_A	J_B	K_B
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

ANALYSIS OF CLOCKED SEQUENTIAL CIRCUITS


Analysis with JK Flip – Flops

 

Present State		I/P	Next State		Flip – Flop Inputs			
A	B	x	A	B	J _A	K _A	J _B	K _B
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

ANALYSIS OF CLOCKED SEQUENTIAL CIRCUITS

Analysis with T Flip – Flops

 

- $T_A = B.x$ $T_B = x$
- $y = A . B$
- $Q(t+1) = T \oplus Q = T'Q + TQ'$
- $A(t+1) = T_A \oplus A = T_A' A + T_A A'$
 $= (Bx)' A + BxA'$
 $= (B' + x')A + A'Bx$
 $= AB' + Ax' + A'Bx$
- $B(t+1) = T_B \oplus B = T_B' B + T_B B'$
 $= x'B + xB'$
 $= x \oplus B$

ANALYSIS OF CLOCKED SEQUENTIAL CIRCUITS


Analysis with T Flip – Flops

- $T_A = B.x$ $T_B = x$
- $y = A . B$
- $Q(t+1) = T \oplus Q = T'Q + TQ'$
- $A(t+1) = T_A \oplus A = T_A' A + T_A A'$
 $= (Bx)' A + BxA'$
 $= (B' + x')A + A'Bx$
 $= \mathbf{AB'} + \mathbf{Ax'} + \mathbf{A'Bx}$
- $B(t+1) = T_B \oplus B = T_B' B + T_B B'$
 $= x'B + xB'$
 $= \mathbf{x \oplus B}$

Present State		I/P	Next State		FF Inputs		Output
A	B	x	A	B	T_A	T_B	y
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	0	1	0	0	0
0	1	1	1	0	1	1	0
1	0	0	1	0	0	0	0
1	0	1	1	1	0	1	0
1	1	0	1	1	0	0	1
1	1	1	0	0	1	1	1

ANALYSIS OF CLOCKED SEQUENTIAL CIRCUITS

Analysis with T Flip – Flops

 

Present State		I/P	Next State		FF Inputs		Output
A	B	x	A	B	T _A	T _B	y
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	0	1	0	0	0
0	1	1	1	0	1	1	0
1	0	0	1	0	0	0	0
1	0	1	1	1	0	1	0
1	1	0	1	1	0	0	1
1	1	1	0	0	1	1	1



5.6 DESIGN PROCEDURE

DESIGN PROCEDURE



- The design of a clocked sequential circuit starts from
 - a set of specifications and
 - culminates in a logic diagram or
 - a list of Boolean functions from which the logic diagram can be obtained.

DESIGN PROCEDURE


1. Derive a state diagram for the circuit from the word description.
2. Reduce the number of states if necessary.
3. Assign binary values to the states.
4. Obtain the binary-coded state table.
5. Choose the type of flip-flops.
6. Derive the simplified flip-flop input equations and output equations.
7. Draw the logic diagram.

DESIGN PROCEDURE

  - Example: We wish to design a circuit that detects three or more consecutive 1's in a string of bits coming through an input line.
- State diagram:




DESIGN PROCEDURE

 

- This is a Moore model sequential circuit since the output is 1 when the circuit is in State3 and 0 otherwise.

State	A	B
S_0	0	0
S_1	0	1
S_2	1	0
S_3	1	1

DESIGN PROCEDURE

 

Present State		I/P	Next State		O/P
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

DESIGN PROCEDURE

- To implement the circuit,
 - Two D flip-flops are chosen to represent the four states and label their outputs A and B.
 - There is one input x.
 - There is one output y.
 - The characteristic equation of the D flip – flop is
 - $Q(t+1) = DQ$.

DESIGN PROCEDURE

- To implement the circuit,
 - The flip – flop input equations can be obtained directly from the next – state columns of A and B and expressed in sum of minterms.
 - $A(t+1) = D_A(A,B,x) = \sum (3, 5, 7)$
 - $B(t+1) = D_B(A,B,x) = \sum (1, 5, 7)$
 - $y(A,B,x) = \sum (6, 7)$

Present State		I/P	Next State		O/P
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

DESIGN PROCEDURE

- Synthesis using D Flip - flops
 - $A(t+1) = D_A(A,B,x) = \sum (3, 5, 7)$
 - $B(t+1) = D_B(A,B,x) = \sum (1, 5, 7)$
 - $y(A,B,x) = \sum (6, 7)$

- D_A 's K - Map

		Bx		B	
A	0	0 0	0 1	1 1	1 0
	0	m_0	m_1	m_3 1	m_2
A	1	m_4	m_5 1	m_7 1	m_6
	1				
				x	

$$D_A = Ax + Bx$$

DESIGN PROCEDURE

- Synthesis using D Flip – flops
 - $A(t+1) = D_A(A,B,x) = \sum (3, 5, 7)$
 - $B(t+1) = D_B(A,B,x) = \sum (1, 5, 7)$
 - $y(A,B,x) = \sum (6, 7)$

- D_B 's K - Map

		B			
		<hr/>			
		0 0	0 1	1 1	1 0
A	0	m_0	m_1 1	m_3	m_2
	1	m_4	m_5 1	m_7 1	m_6
		<hr/>			
		x			

$$D_A = Ax + B'x$$

DESIGN PROCEDURE

- Synthesis using D Flip – flops
 - $A(t+1) = D_A(A,B,x) = \sum (3, 5, 7)$
 - $B(t+1) = D_B(A,B,x) = \sum (1, 5, 7)$
 - $y(A,B,x) = \sum (6, 7)$

- y's K - Map

		B			
		0 0	0 1	1 1	1 0
A	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7 1	m_6 1

x

$$y = AB$$

DESIGN PROCEDURE


- Synthesis using D Flip – flops

- $D_A = Ax + Bx$

- $D_B = Ax + B'x$

- $y = AB$

- Logic Diagram of Sequence

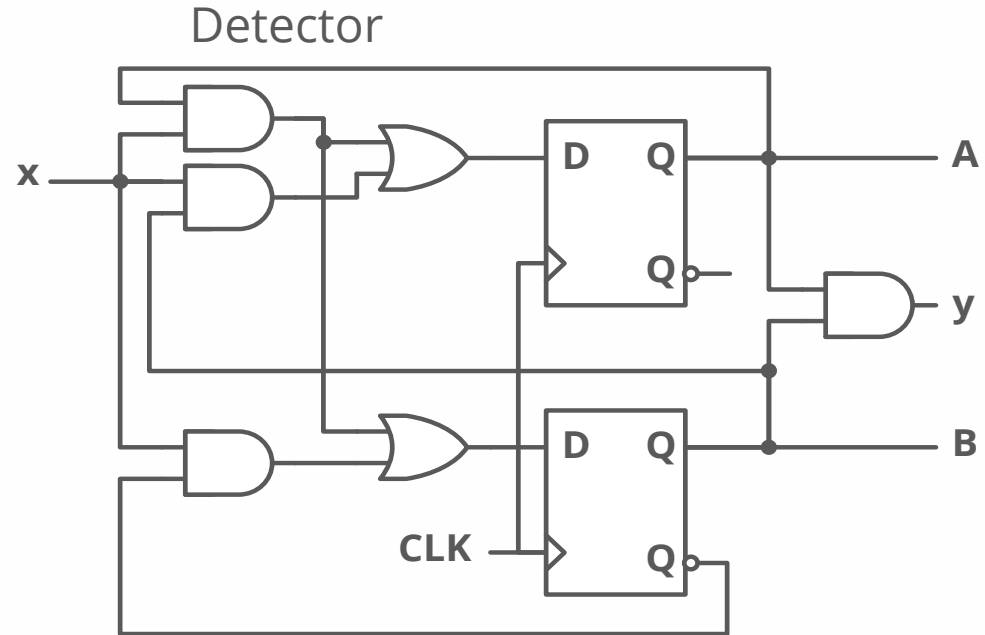

DESIGN PROCEDURE

- When – D type flip-flops are employed, the input equations are obtained directly from the next state.
- This is not the case for the JK and T types of flip-flops. In order to determine the input equations for these flip flops, it is necessary to derive a functional relationship between the state table and the input equations.

DESIGN PROCEDURE

- During the design process we usually know the transition from present state to the next state and wish to find the flip – flop input conditions that will cause the required transition.
- For this reason, we need a table that lists the required inputs for a given change of state. Such table is called an **excitation table**.

DESIGN PROCEDURE

- D Flip – Flop Excitation table

D Flip – Flop Characteristic Table

D	Q (t+1)
0	0
1	1

$$Q(t+1) = D$$

Present State	Next State	F.F. Input
Q(t)	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1

DESIGN PROCEDURE

- JK Flip – Flop Excitation table

JK Flip – Flop Characteristic Table

J	K	Q (t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	Q'(t)

$$Q(t+1) = JQ' + K'Q$$

Present State	Next State	F.F. Input	
Q(t)	Q(t+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

0 0 (No change)
0 1 (Reset)

1 0 (Set)
1 1 (Toggle)

0 1 (Reset)
1 1 (Toggle)

0 0 (No change)
1 0 (Set)

DESIGN PROCEDURE

- T Flip – Flop Excitation table

T Flip – Flop Characteristic Table


T	Q (t+1)
0	Q(t)
1	Q'(t)

$$Q(t+1) = T \oplus Q$$

Present State	Next State	F.F. Input
Q(t)	Q(t+1)	T
0	0	0
0	1	1
1	0	1
1	1	0

DESIGN PROCEDURE

 - Synthesis Using JK Flip – Flops: Detect 3 or more consecutive 1's



DESIGN PROCEDURE

- Synthesis Using JK Flip – Flops: Detect 3 or more consecutive 1's

Present State		Input	Next State		Flip-Flop Inputs			
A	B		A	B	J_A	K_A	J_B	K_B
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	0	0	0	X	X	1
0	1	1	1	0	1	X	X	1
1	0	0	0	0	X	1	0	X
1	0	1	1	1	X	0	1	X
1	1	0	0	0	X	1	X	1
1	1	1	1	1	X	0	X	0

$$J_A(A, B, x) = \sum (3, 4, 5, 6, 7)$$

$$K_A(A, B, x) = \sum (0, 1, 2, 3, 4, 6)$$

$$J_B(A, B, x) = \sum (1, 2, 3, 5, 6, 7)$$

$$K_B(A, B, x) = \sum (0, 1, 2, 3, 4, 5, 6)$$

DESIGN PROCEDURE

- Synthesis Using JK Flip – Flops:

Detect 3 or more consecutive 1's

- $J_A(A, B, x) = \sum (3, 4, 5, 6, 7)$
- $K_A(A, B, x) = \sum (0, 1, 2, 3, 4, 6)$
- $J_B(A, B, x) = \sum (1, 2, 3, 5, 6, 7)$
- $K_B(A, B, x) = \sum (0, 1, 2, 3, 4, 5, 6)$

- J_A 's K-Map

		B			
		Bx		1 1	1 0
A	0	m_0	m_1	m_3 1	m_2
	1	m_4 X	m_5 X	m_7 X	m_6 X

X

$$J_A = Bx$$

DESIGN PROCEDURE

- Synthesis Using JK Flip – Flops:

Detect 3 or more consecutive 1's

- $J_A(A, B, x) = \sum (3, 4, 5, 6, 7)$
- $K_A(A, B, x) = \sum (0, 1, 2, 3, 4, 6)$
- $J_B(A, B, x) = \sum (1, 2, 3, 5, 6, 7)$
- $K_B(A, B, x) = \sum (0, 1, 2, 3, 4, 5, 6)$

- K_A 's K-Map

		B			
		00	01	11	10
A	0	m_0 X	m_1 X	m_3 X	m_2 X
	1	m_4 1	m_5	m_7	m_6 1

X

$$K_A = x'$$

DESIGN PROCEDURE

- Synthesis Using JK Flip – Flops:

Detect 3 or more consecutive 1's

- $J_A(A, B, x) = \sum (3, 4, 5, 6, 7)$
- $K_A(A, B, x) = \sum (0, 1, 2, 3, 4, 6)$
- $J_B(A, B, x) = \sum (1, 2, 3, 5, 6, 7)$
- $K_B(A, B, x) = \sum (0, 1, 2, 3, 4, 5, 6)$

- J_B 's K-Map

		B			
		00	01	11	10
A	0	m_0	m_1 1	m_3 X	m_2 X
	1	m_4	m_5 1	m_7 X	m_6 X

X

$J_B = X$

DESIGN PROCEDURE

- Synthesis Using JK Flip – Flops:

Detect 3 or more consecutive 1's

- $J_A(A, B, x) = \sum (3, 4, 5, 6, 7)$
- $K_A(A, B, x) = \sum (0, 1, 2, 3, 4, 6)$
- $J_B(A, B, x) = \sum (1, 2, 3, 5, 6, 7)$
- $K_B(A, B, x) = \sum (0, 1, 2, 3, 4, 5, 6)$

- K_B 's K-Map

		B			
		00	01	11	10
A	0	m_0 X	m_1 X	m_3 1	m_2 1
	1	m_4 X	m_5 X	m_7	m_6 1


X

$$K_B = A' + x'$$

DESIGN PROCEDURE


- Synthesis Using JK Flip – Flops:
Detect 3 or more consecutive 1's
 - $J_A = Bx$
 - $K_A = x'$
 - $J_B = x$
 - $K_B = A' + x'$

- Logic Diagram of Sequence Detector

 

DESIGN PROCEDURE

 - Synthesis Using T Flip – Flops: 3-bit Counter. An n-bit binary counter consists of n flip – flops that can count in binary from 0 to $2^n - 1$.



DESIGN PROCEDURE

- Synthesis Using T Flip – Flops: 3-bit Counter.

Present State			Next State			Flip-Flop Inputs		
A_2	A_1	A_0	A_2	A_1	A_0	T_{A2}	T_{A1}	T_{A0}
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

$$T_{A2}(A_2, A_1, A_0) = \sum (3, 7)$$

$$T_{A1}(A_2, A_1, A_0) = \sum (1, 3, 5, 7)$$

$$T_{A0}(A_2, A_1, A_0) = \sum (0, 1, 2, 3, 4, 5, 6, 7)$$

DESIGN PROCEDURE

- Synthesis Using T Flip – Flops: 3-bit Counter.

- $T_{A2}(A_2, A_1, A_0) = \Sigma(3, 7)$
- $T_{A1}(A_2, A_1, A_0) = \Sigma(1, 3, 5, 7)$
- $T_{A0}(A_2, A_1, A_0) = \Sigma(0, 1, 2, 3, 4, 5, 6, 7)$

- T_{A2} 's K-Map

		A_1A_0			
				A_1	
A_2	A	0 0	0 1	1 1	1 0
		m_0	m_1	m_3	m_2
0				1	
1		m_4	m_5	m_7	m_6
				1	
				A_0	

$$T_{A2} = A_1A_0$$

DESIGN PROCEDURE

- Synthesis Using T Flip – Flops: 3-bit Counter.

- $T_{A2}(A_2, A_1, A_0) = \Sigma(3, 7)$
- $T_{A1}(A_2, A_1, A_0) = \Sigma(1, 3, 5, 7)$
- $T_{A0}(A_2, A_1, A_0) = \Sigma(0, 1, 2, 3, 4, 5, 6, 7)$

- T_{A1} 's K-Map

		A_1A_0		A_1	
		0 0	0 1	1 1	1 0
A_2	0	m_0	m_1 1	m_3 1	m_2
	1	m_4	m_5 1	m_7 1	m_6
				A_0	

$$T_{A1} = A_0$$

DESIGN PROCEDURE

- Synthesis Using T Flip – Flops: 3-bit Counter.

- $T_{A2}(A_2, A_1, A_0) = \Sigma (3, 7)$
- $T_{A1}(A_2, A_1, A_0) = \Sigma (1, 3, 5, 7)$
- $T_{A0}(A_2, A_1, A_0) = \Sigma (0, 1, 2, 3, 4, 5, 6, 7)$

- T_{A0} 's K-Map

		A_1			
		0 0	0 1	1 1	1 0
A_2	0	m_0 1	m_1 1	m_3 1	m_2 1
	1	m_4 1	m_5 1	m_7 1	m_6 1


$$T_{A0} = 1$$


DESIGN PROCEDURE

- Synthesis Using T Flip – Flops: 3-bit Counter.

- $T_{A2} = A_1 A_0$
- $T_{A1} = A_0$
- $T_{A0} = 1$

- Logic Diagram of 3-bit Binary Counter

 

 

THANK YOU!